

# RF Power Amplifier Design

**Markus Mayer & Holger Arthaber**

Department of Electrical Measurements and Circuit Design

Vienna University of Technology

*June 11, 2001*



# Contents

---


- Basic Amplifier Concepts
  - Class A, B, C, F, hHCA
  - Linearity Aspects
  - Amplifier Example
  
- Enhanced Amplifier Concepts
  - Feedback, Feedforward, ...
  - Predistortion
  - LINC, Doherty, EER, ...

# Efficiency Definitions

• Drain Efficiency:  $\eta_D = \frac{P_{OUT}}{P_{DC}}$


• Power Added Efficiency:  $\eta_{PA} = \frac{P_{OUT} - P_{IN}}{P_{DC}} = \eta_D \cdot \left(1 - \frac{1}{G}\right)$
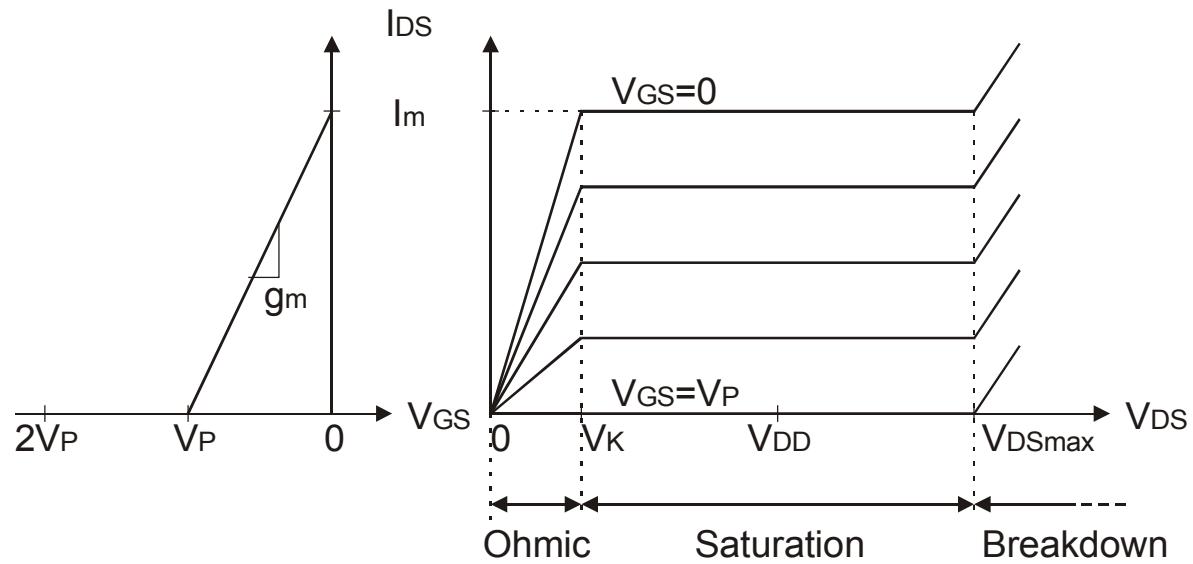
# Ideal FET Input and Output Characteristics




$$\kappa = \frac{V_{DD} - V_K}{V_{DD}}$$

# Maximum Output Power Match

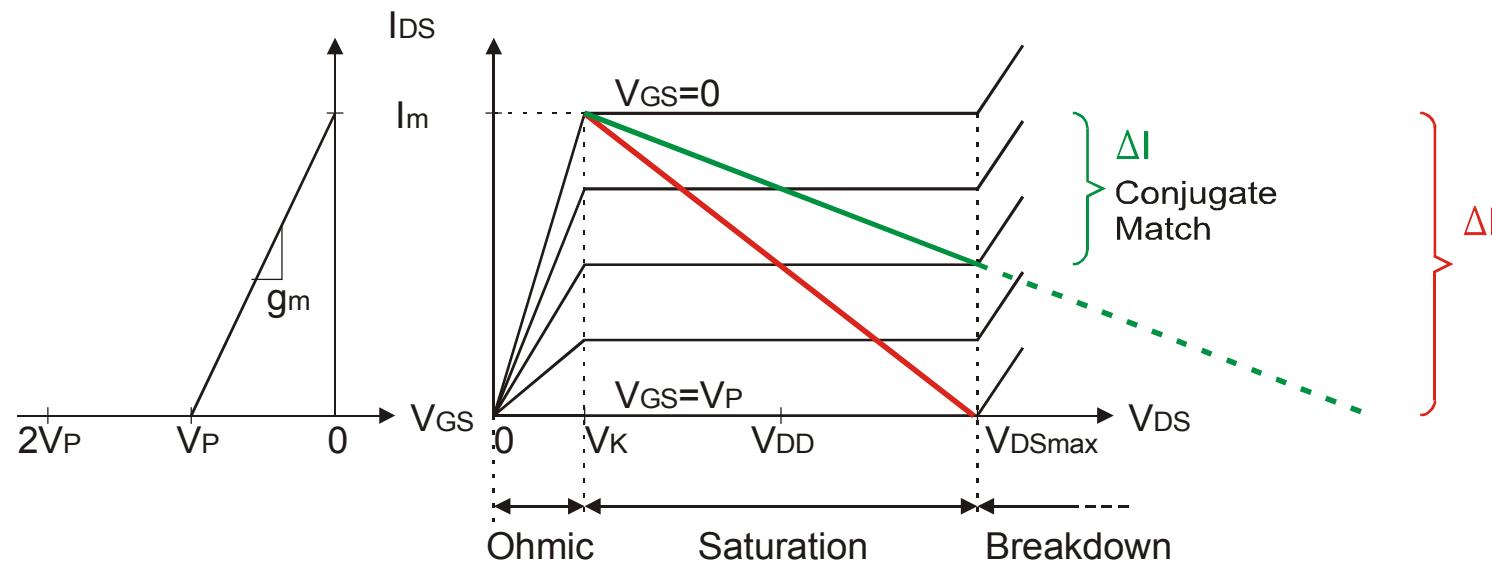


$$R_{OPT} = \frac{V_{DSmax} - V_K}{I_m}$$

# Class A

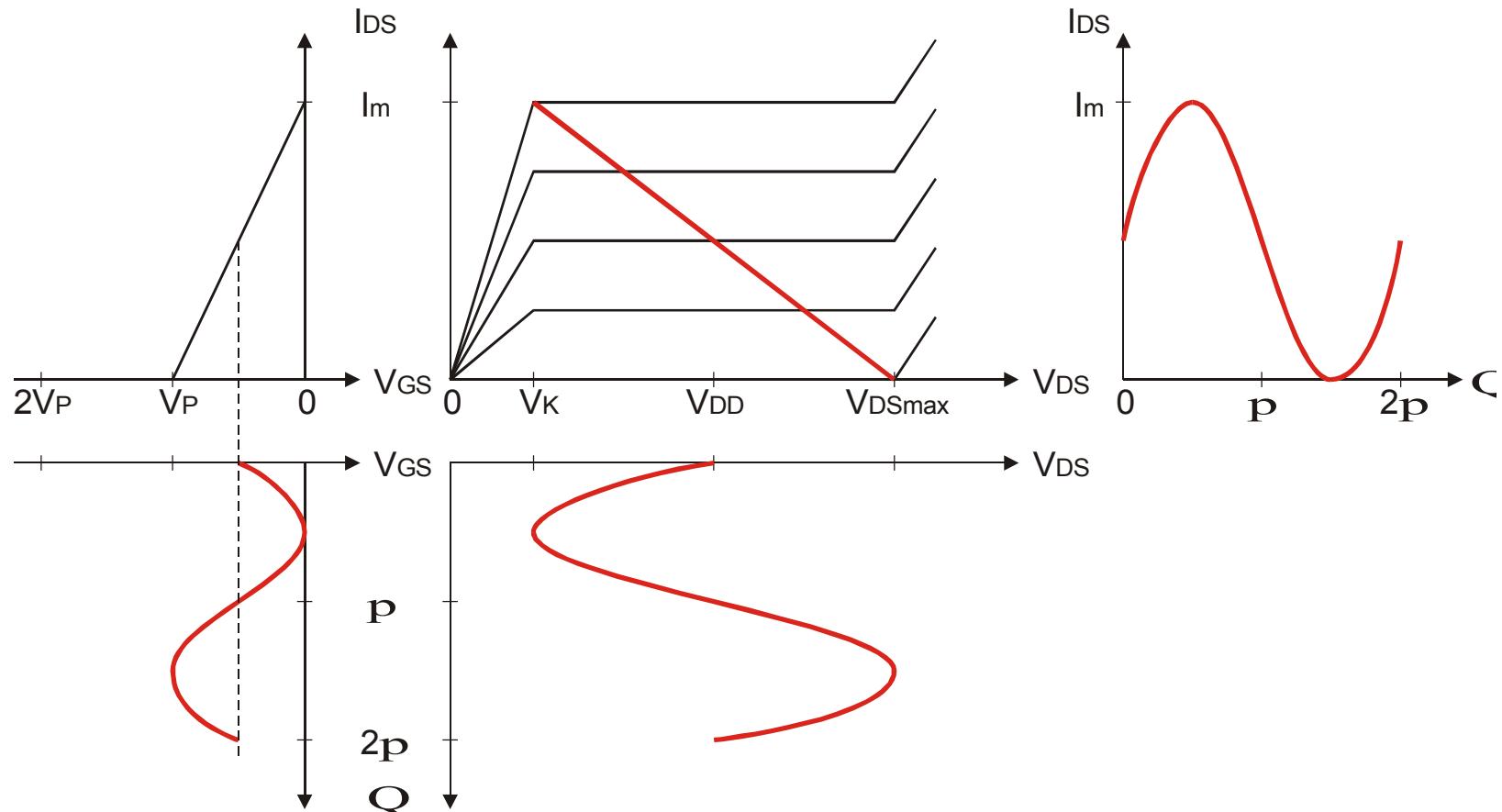

# Class A – Circuit

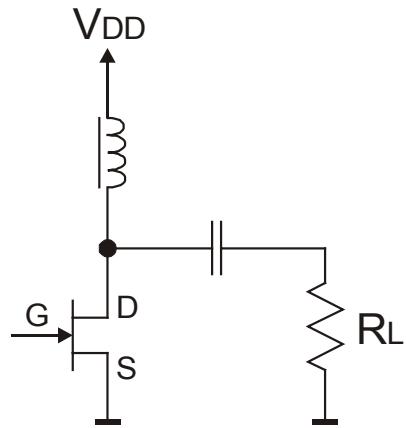


$$\eta_D = \kappa \cdot 50\%$$


$$G = G_A \quad (\text{e.g. } 14 \text{ dB})$$

$$\eta_{PA} = \kappa \cdot 48\%$$


# Class B

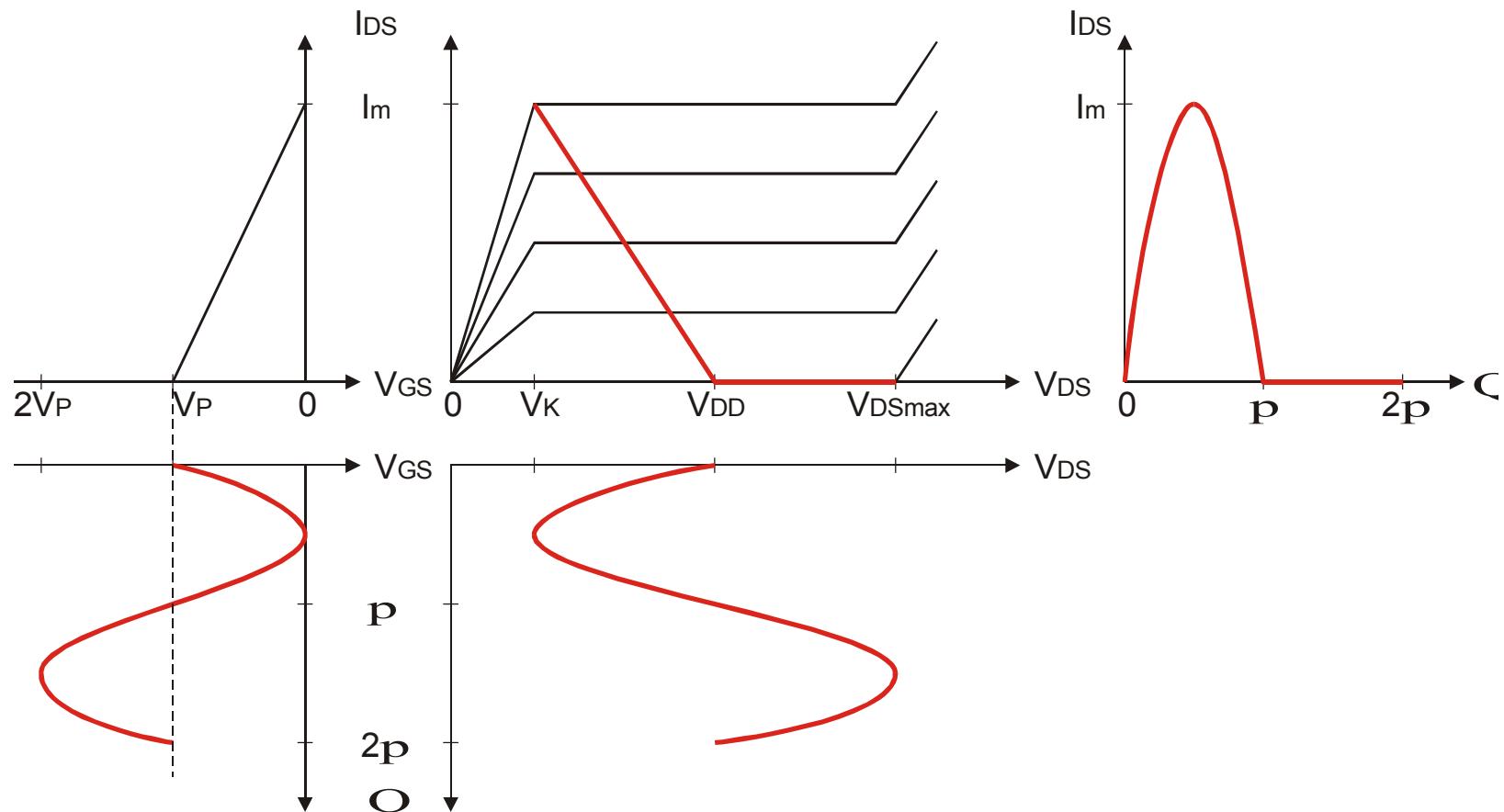

# Class C

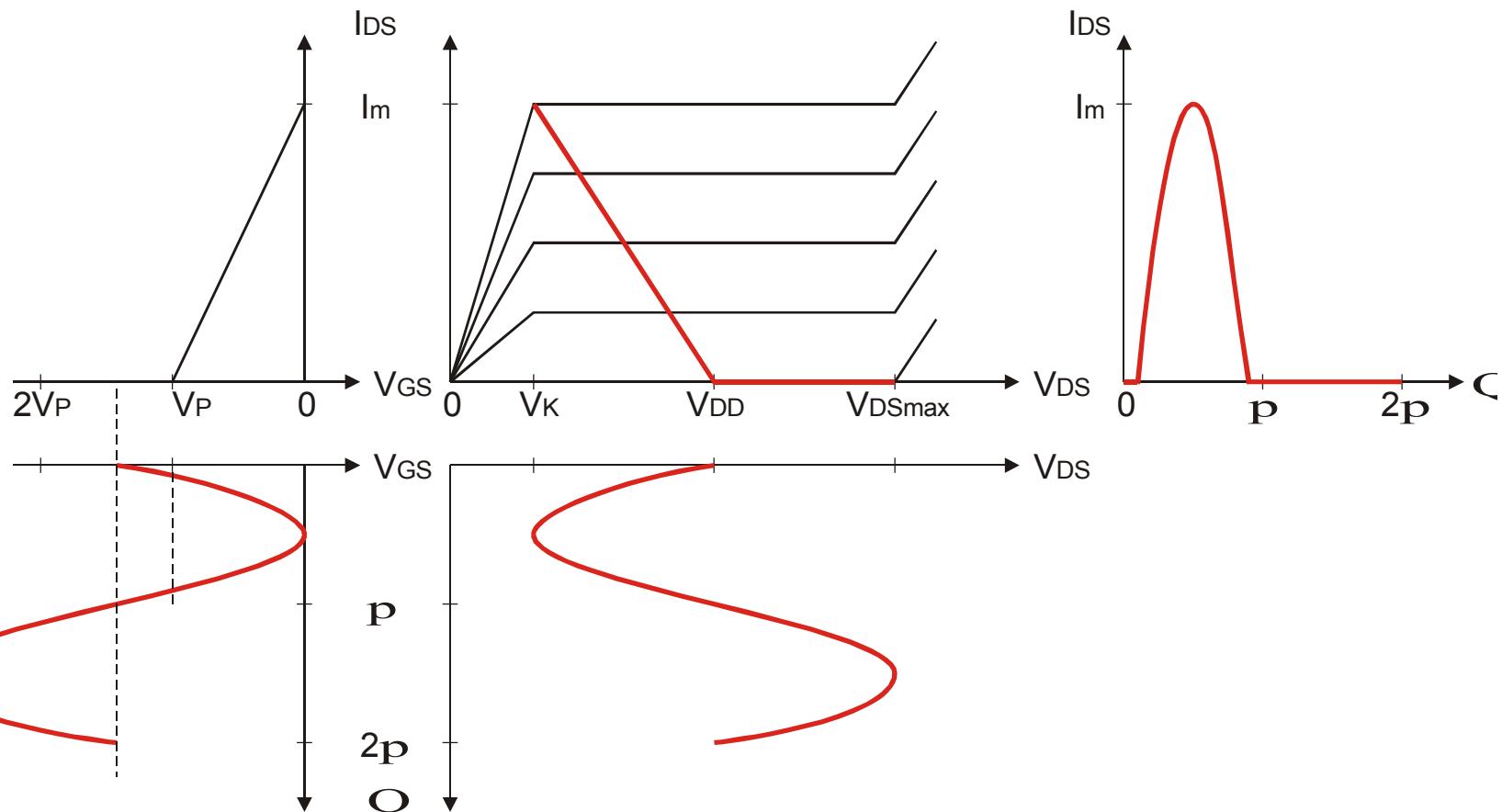

# Class B and C – Circuit

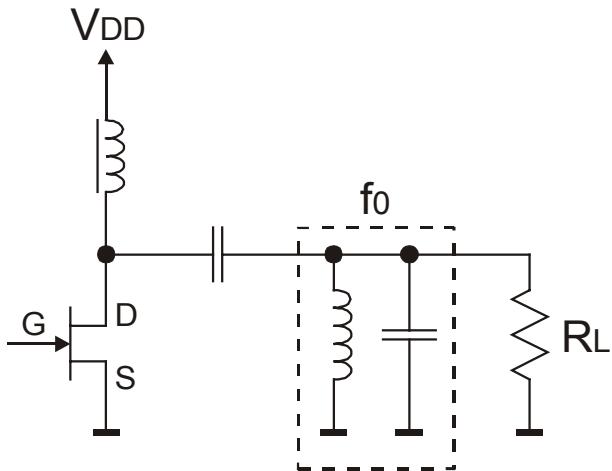

Class B

$$\eta_D = \kappa \cdot 78\%$$

$$G = G_A - 6\text{dB} \quad (8\text{ dB})$$

Class C


$$\eta_D \rightarrow 100\%$$

$$G \rightarrow 1$$


$$\eta_{PA} = \kappa \cdot 65\%$$

$$\eta_{PA} \rightarrow 0\%$$


# Influence of Conduction Angle

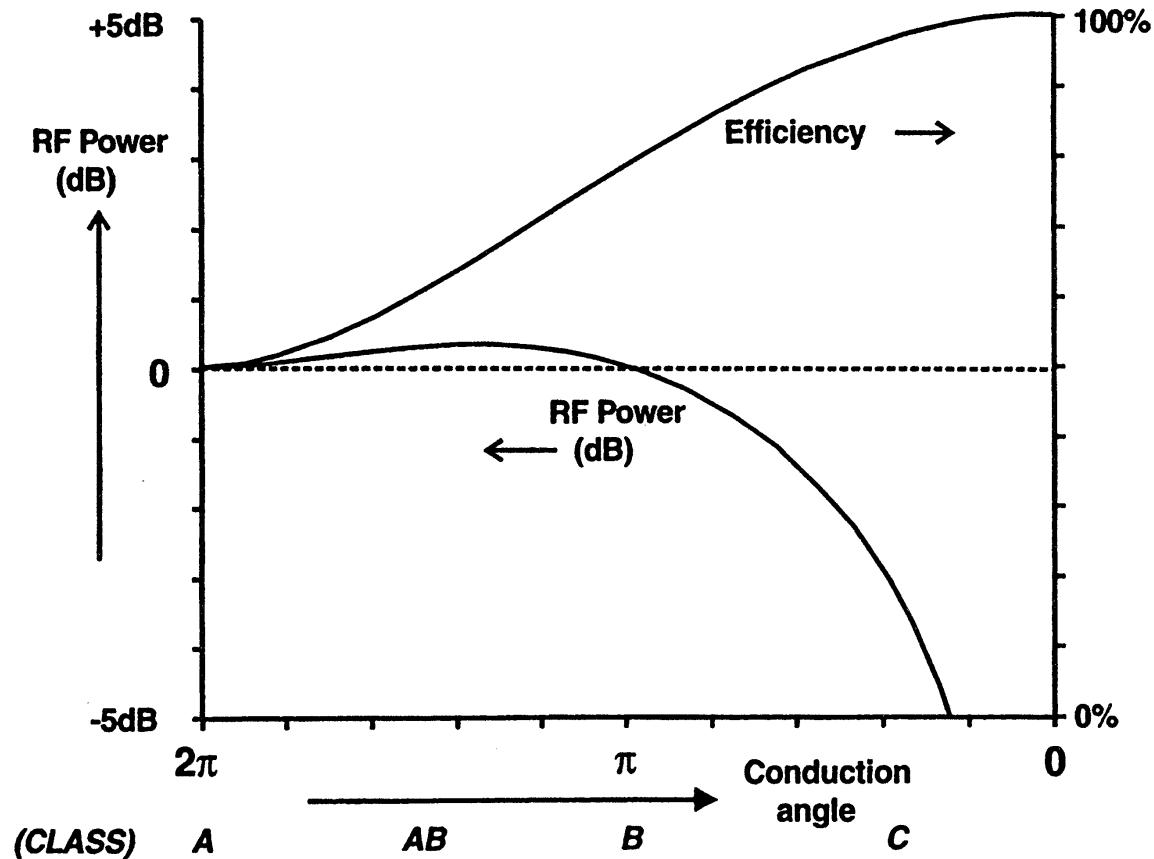

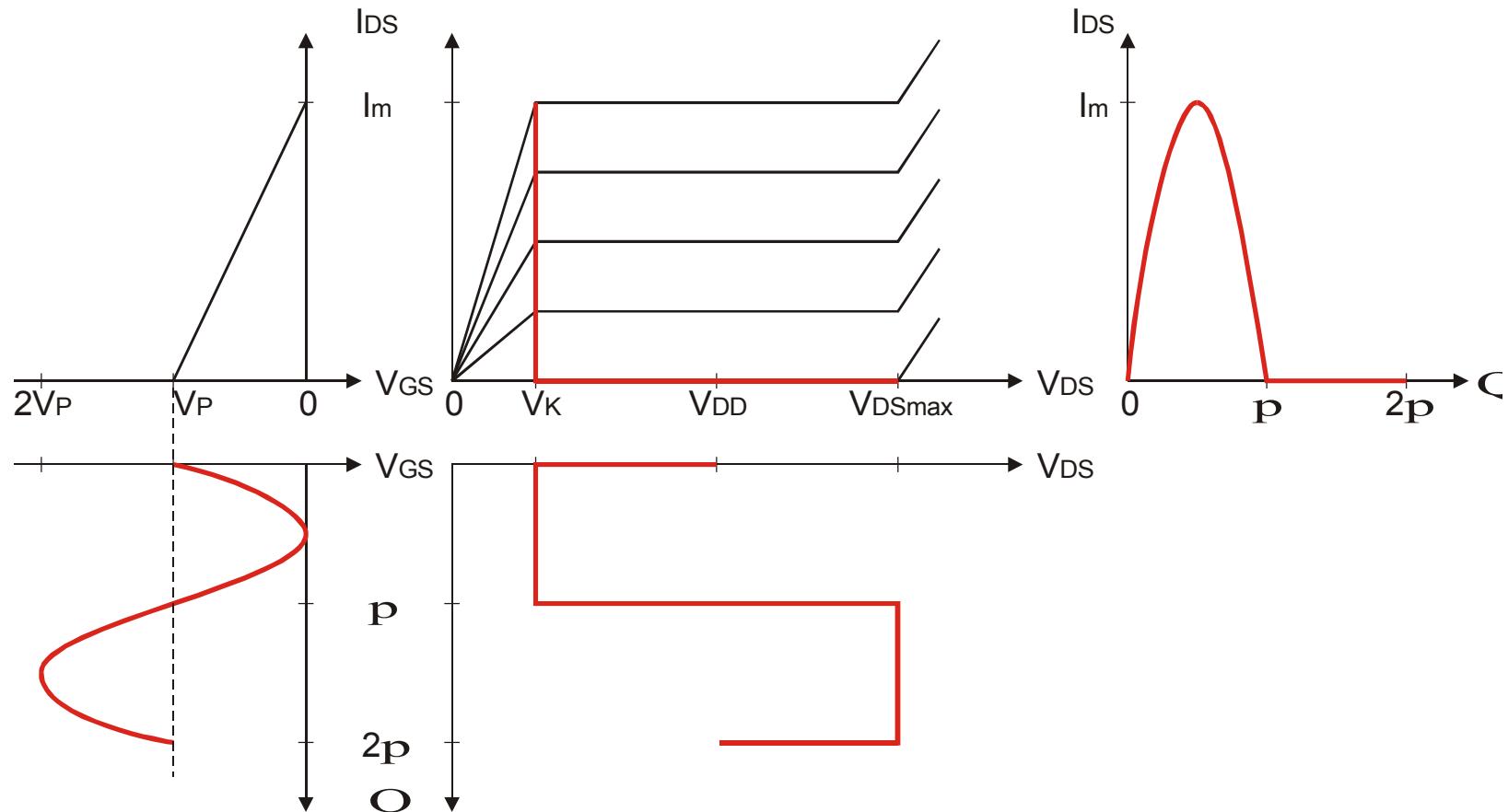
# Class F (HCA ... harmonic controlled amplifier)



# hHCA (half sinusoidally driven HCA)

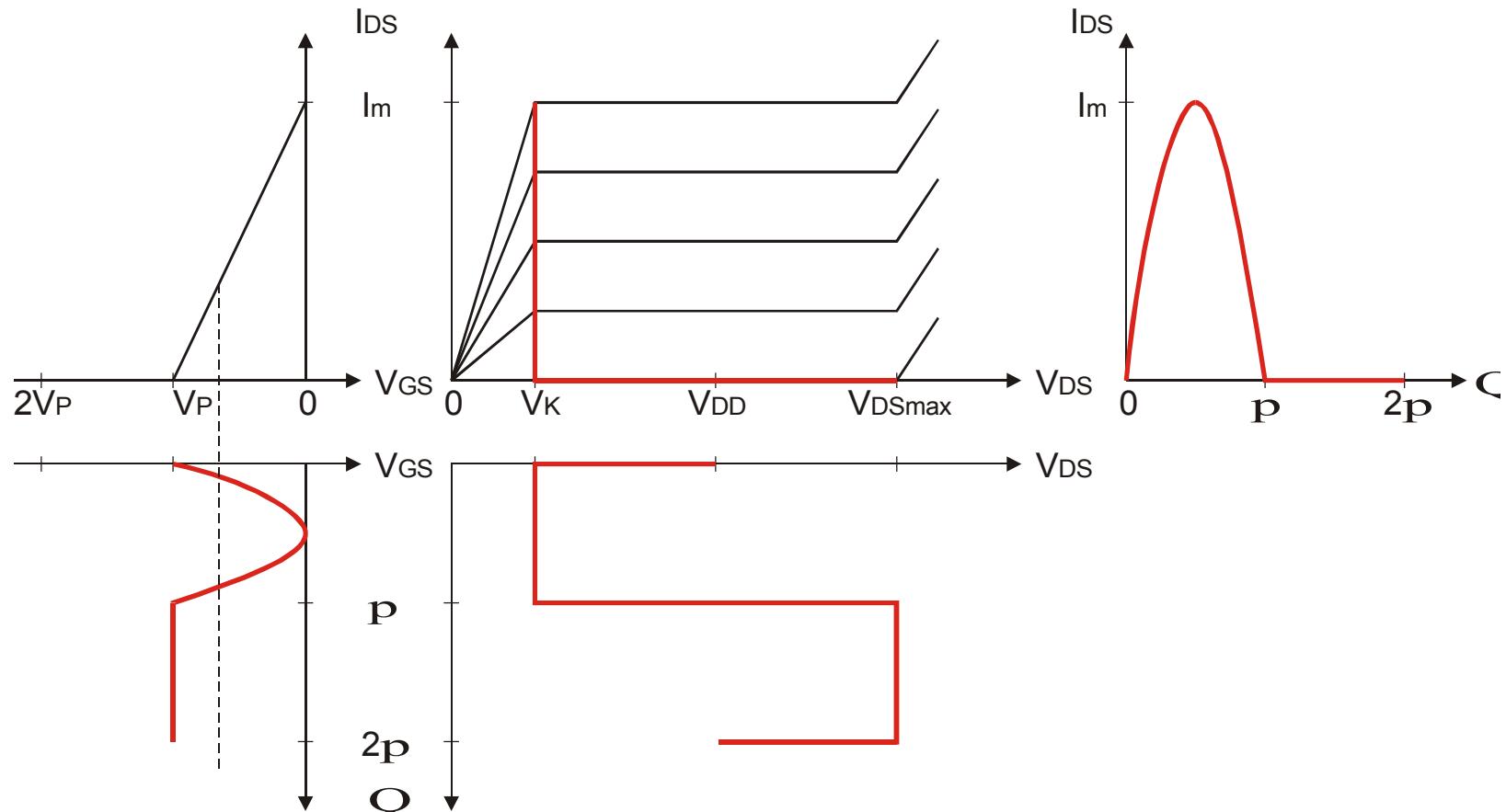

# Class F and hHCA – Circuit

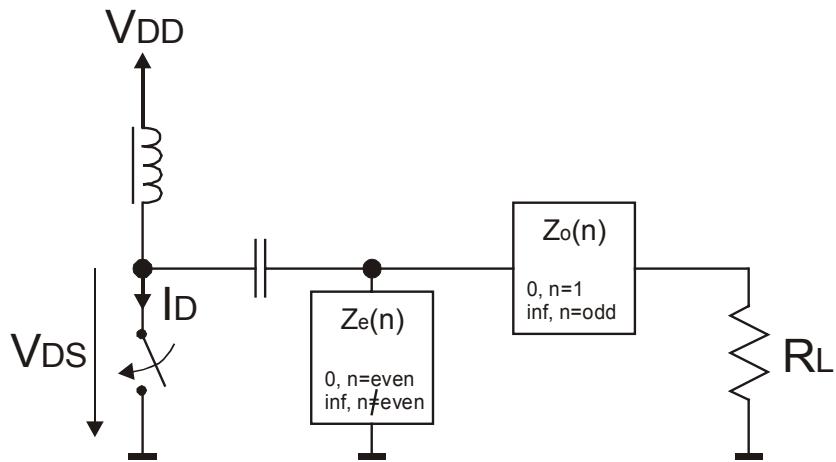

Class F

$$\eta_D = \kappa \cdot 100\%$$

$$G = G_A - 5 \text{ dB} \quad (9 \text{ dB})$$

hHCA


$$\eta_D = \kappa \cdot 100\%$$

$$G = G_A + 1 \text{ dB} \quad (15 \text{ dB})$$


$$\eta_{PA} = \kappa \cdot 87\%$$

$$\eta_{PA} = \kappa \cdot 96\%$$

# hHCA – Third Harmonic Peaking

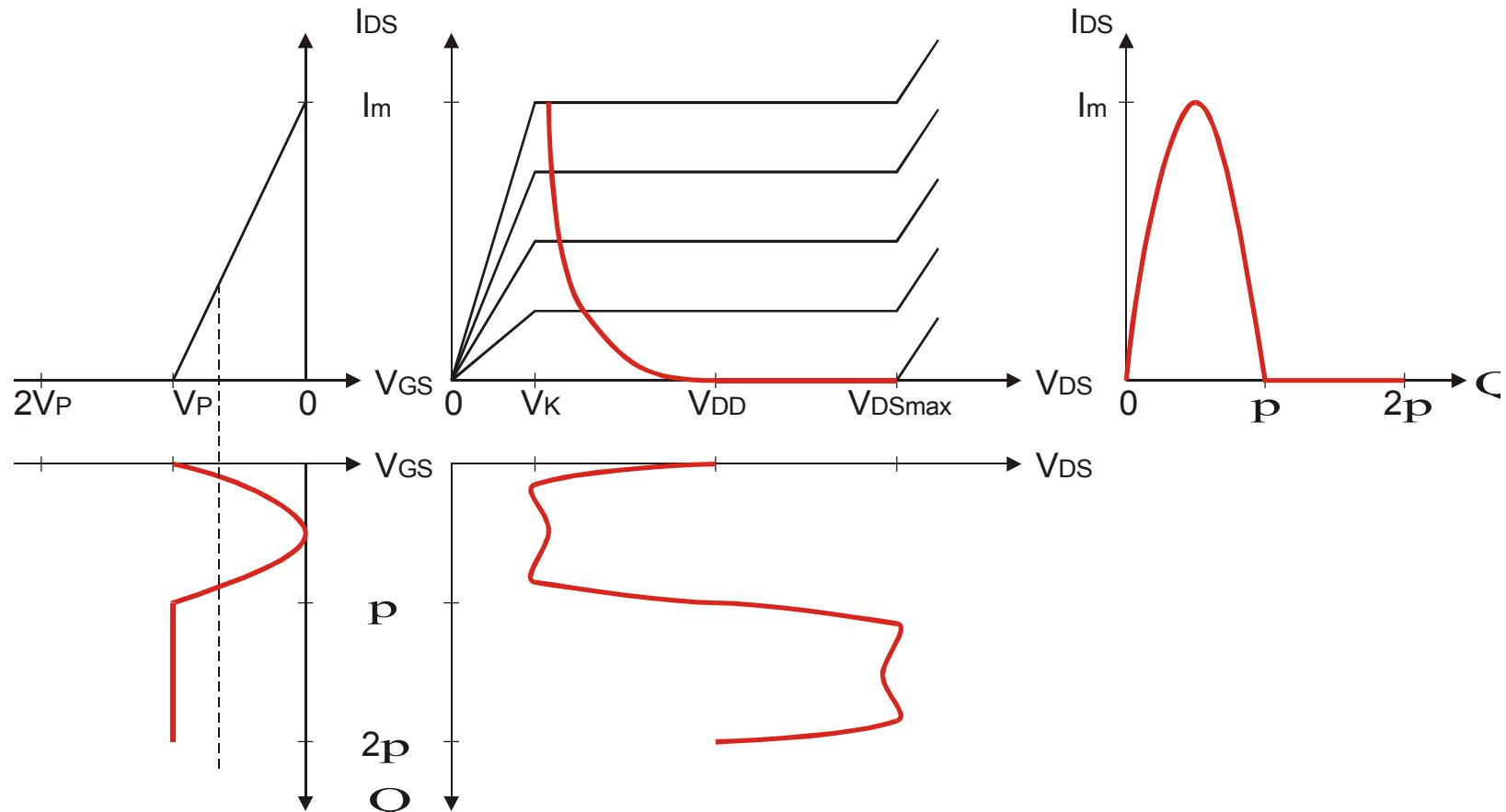

# Third Harmonic Peaking – Circuit

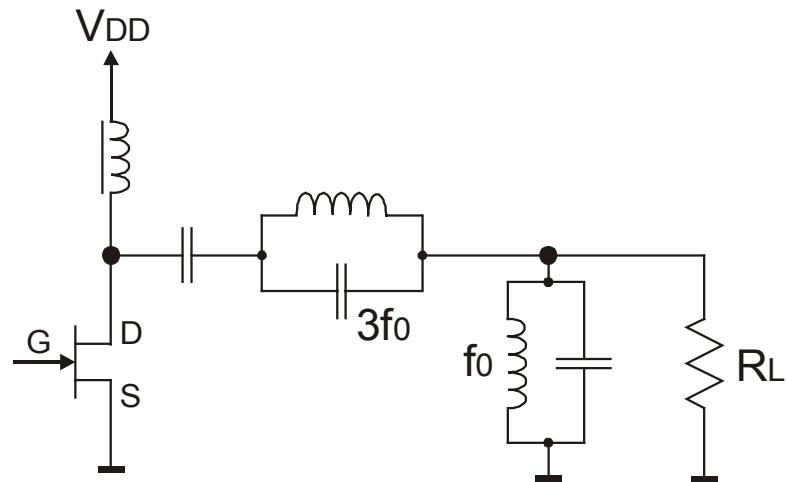


$$\eta_D = \kappa \cdot 91\%$$

$$G = G_A + 0.6 \text{ dB} \quad (14.6 \text{ dB})$$



$$\eta_{PA} = \kappa \cdot 87\%$$

# Linearity Aspects


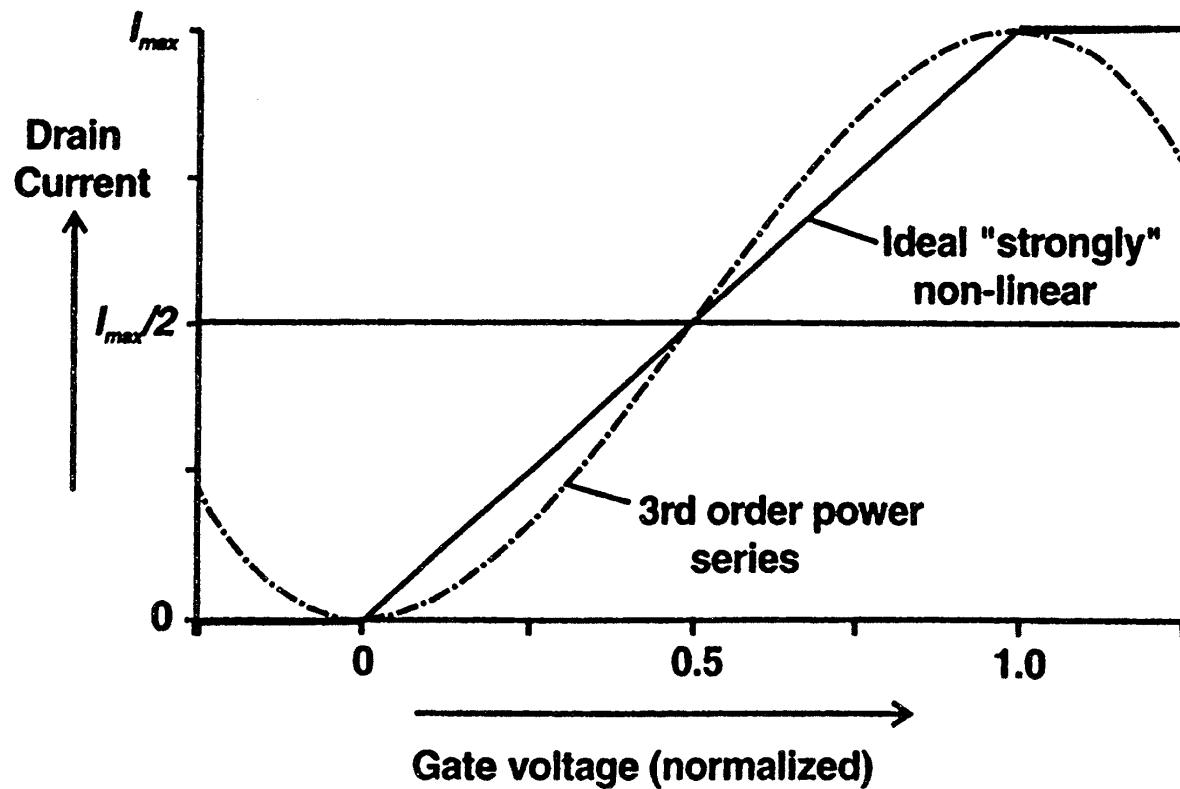


# Linearity Aspects


○ Class A

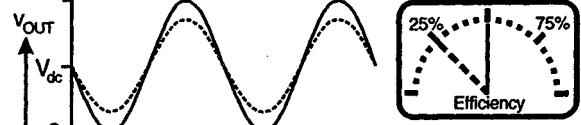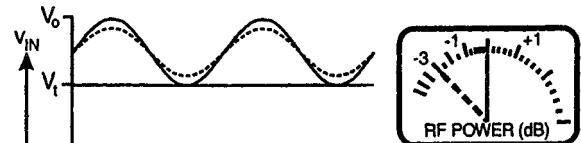




○ Class B

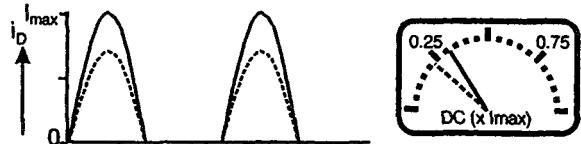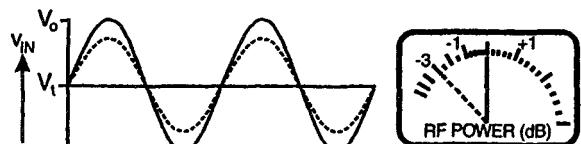



○ Class AB

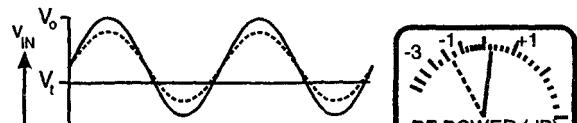

○ Class C

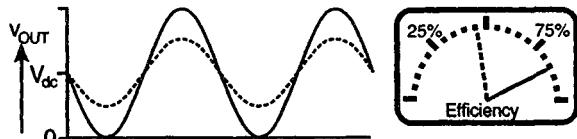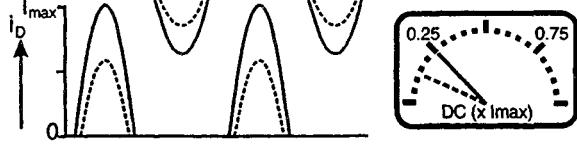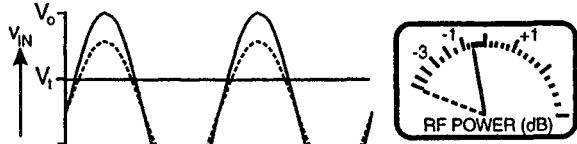

# Linearity Aspects

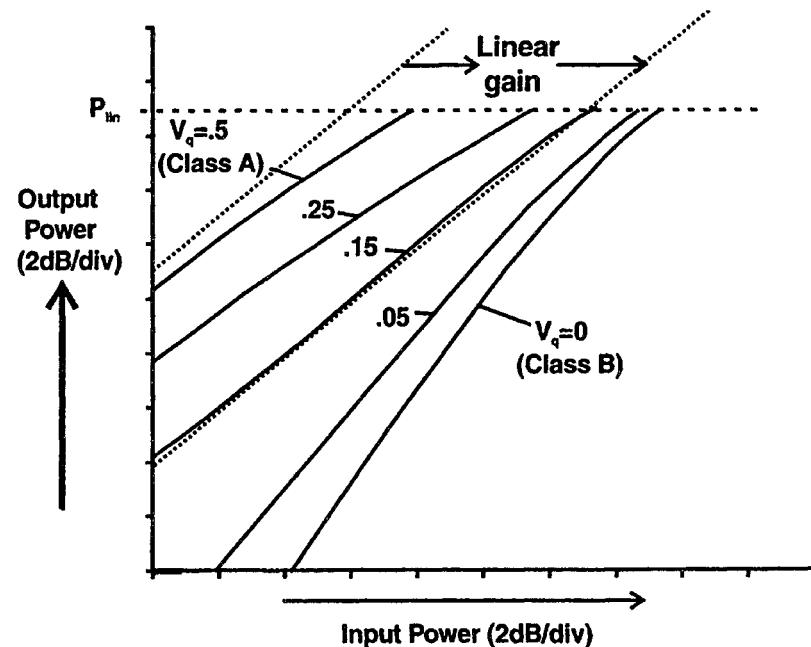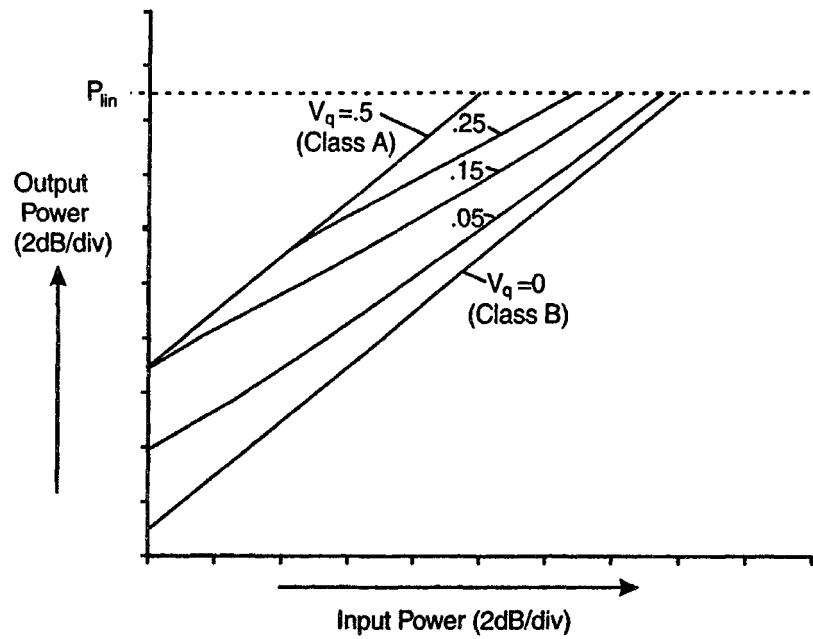


○ Ideal strongly nonlinear model

○ Strong-weak nonlinear model



# Amplifier Design – An Example

## ⑤ Balanced Amplifier Configuration

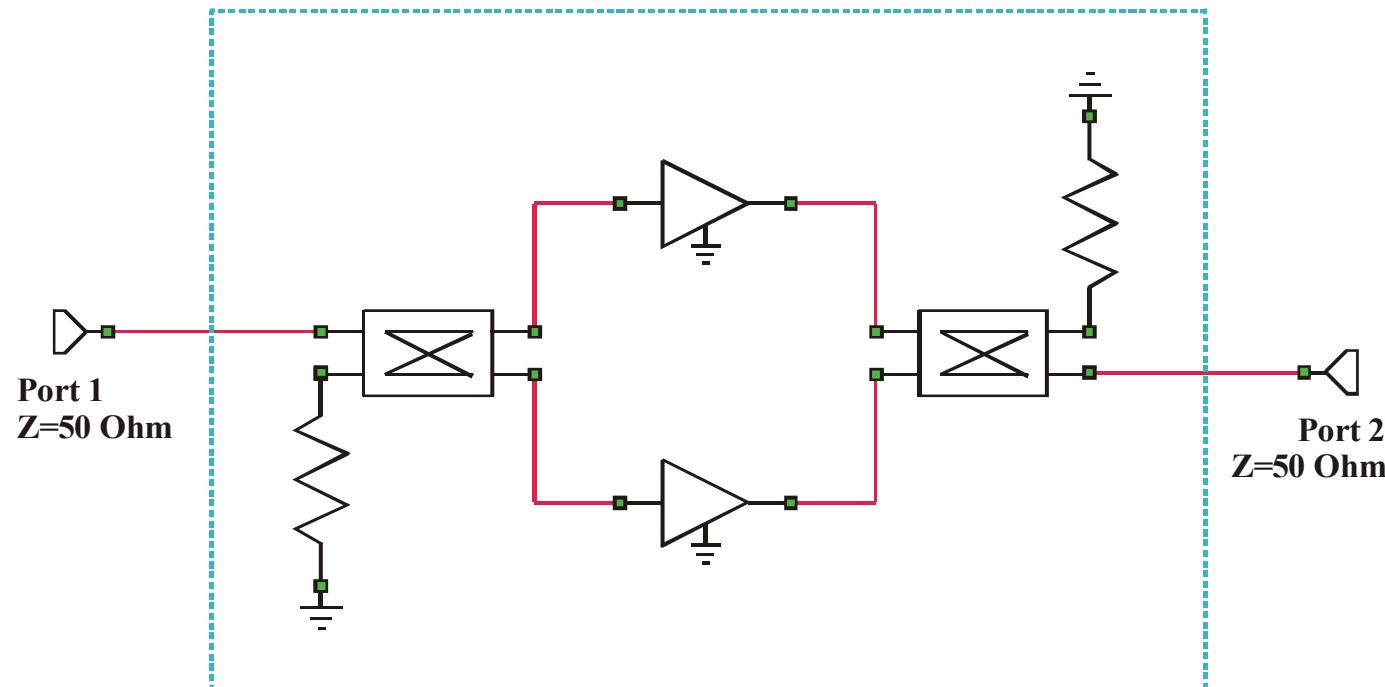



# Amplifier Design – Simulation

## ⦿ Gate & Drain Waveforms

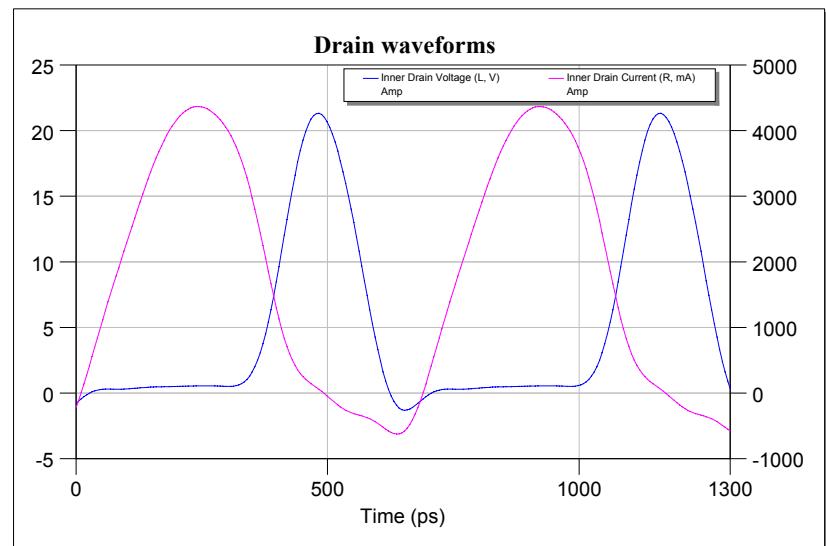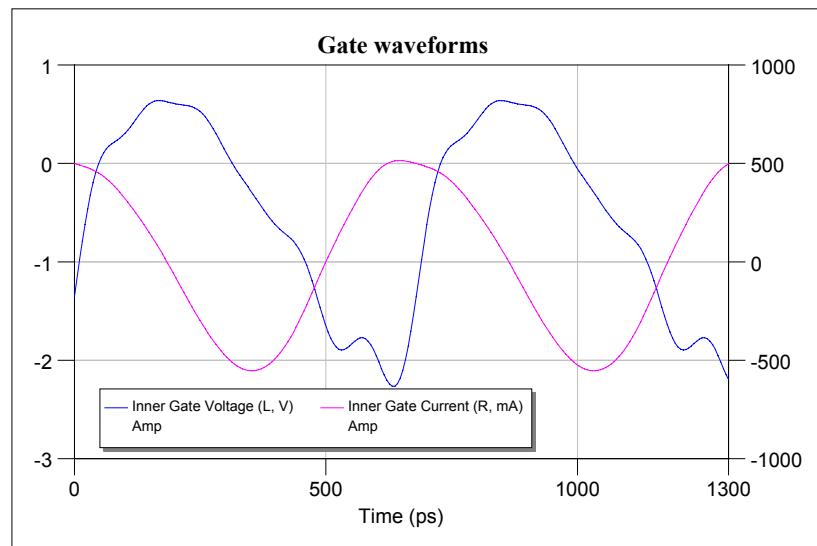



# Amplifier Design – Simulation

## ○ Dynamic Load Line & Power Sweep

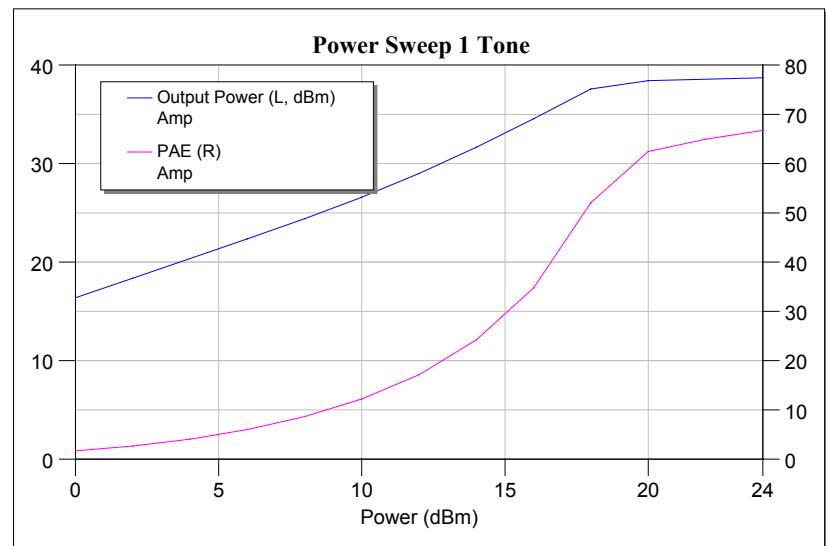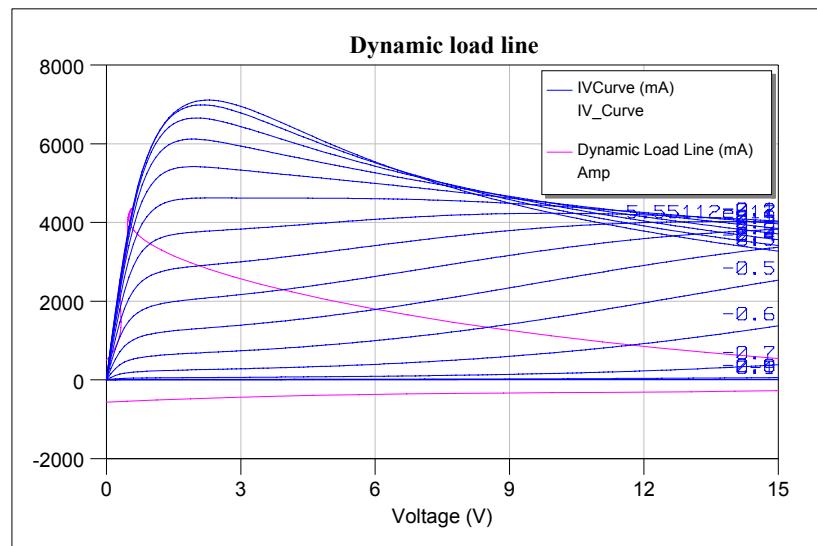



# Amplifier Design – Measurements

## ○ Single Tone & Two Tone

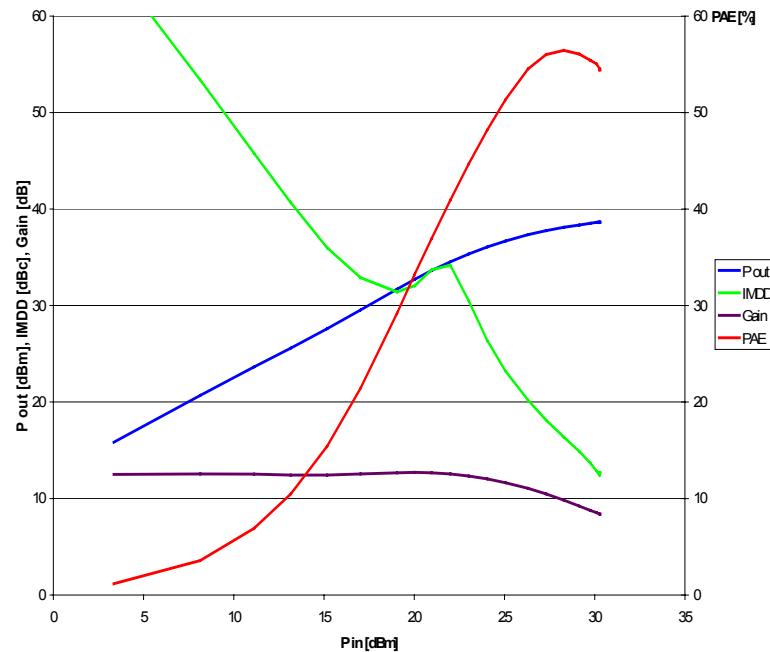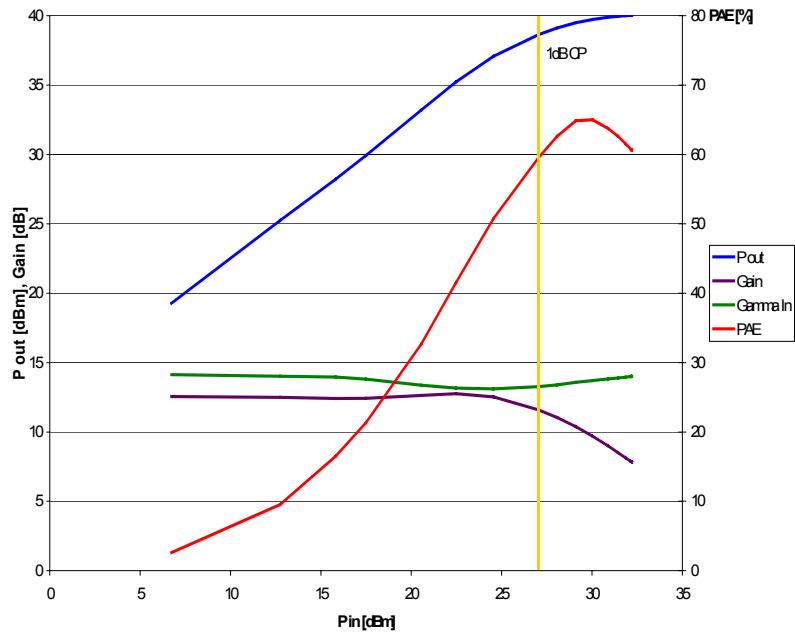

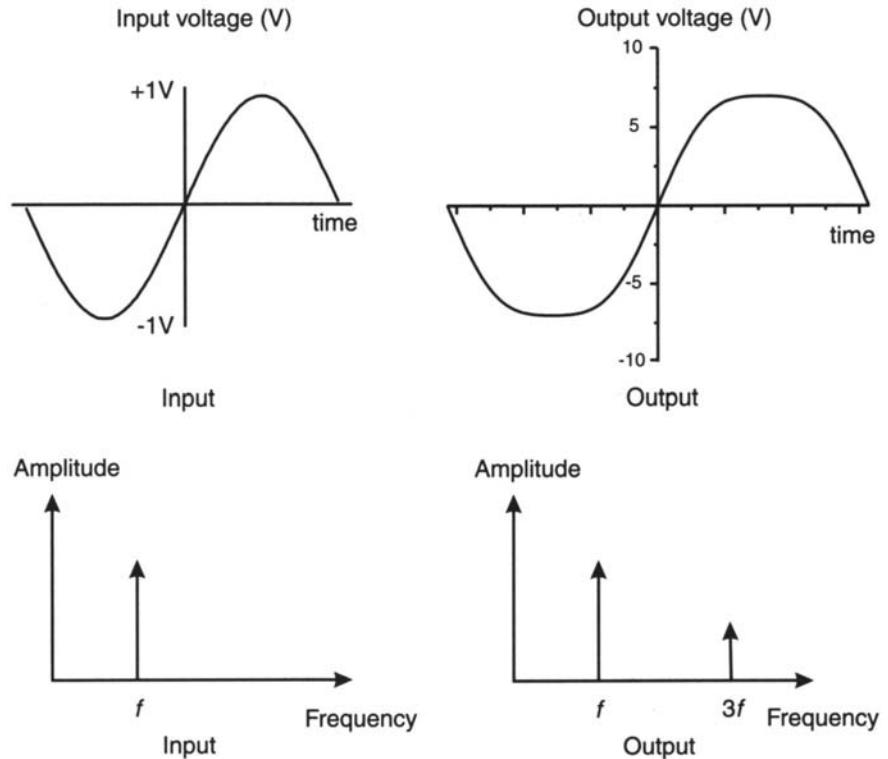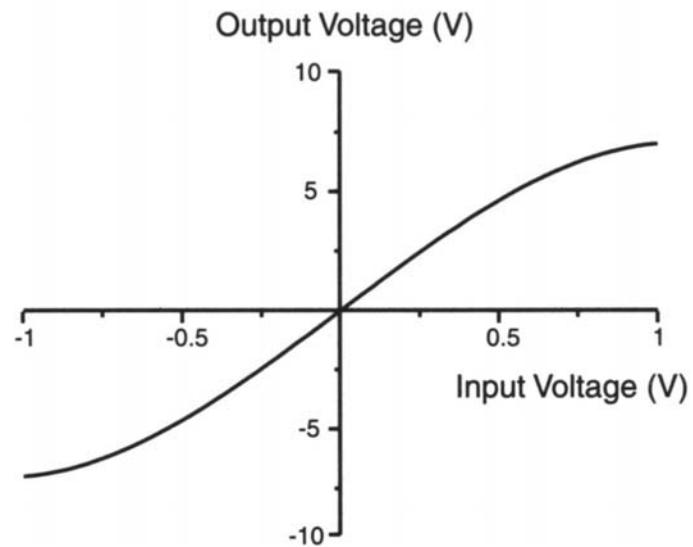
# Amplifier Nonlinearity

- Gain and Phase depends on Input Signal
- 3<sup>rd</sup> Order Gain-Nonlinearities:


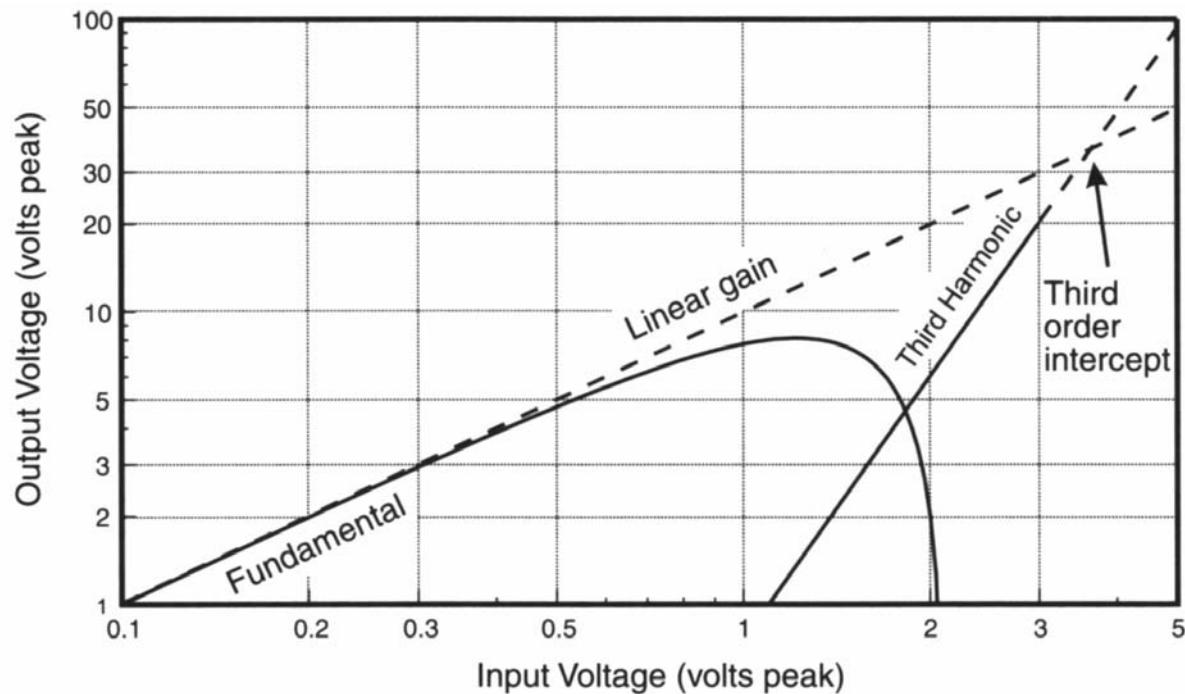
# Amplifier Nonlinearity


- Higher Output Level (close to Saturation) results in more Distortion/Nonlinearity




# Nonlinearity leads to?

- Generation of Harmonics
- Intermodulation Distortion / Spectral Regrowth
- SNR (NPR) Degradation
- Constellation Deformation

# Intermodulation and Harmonics

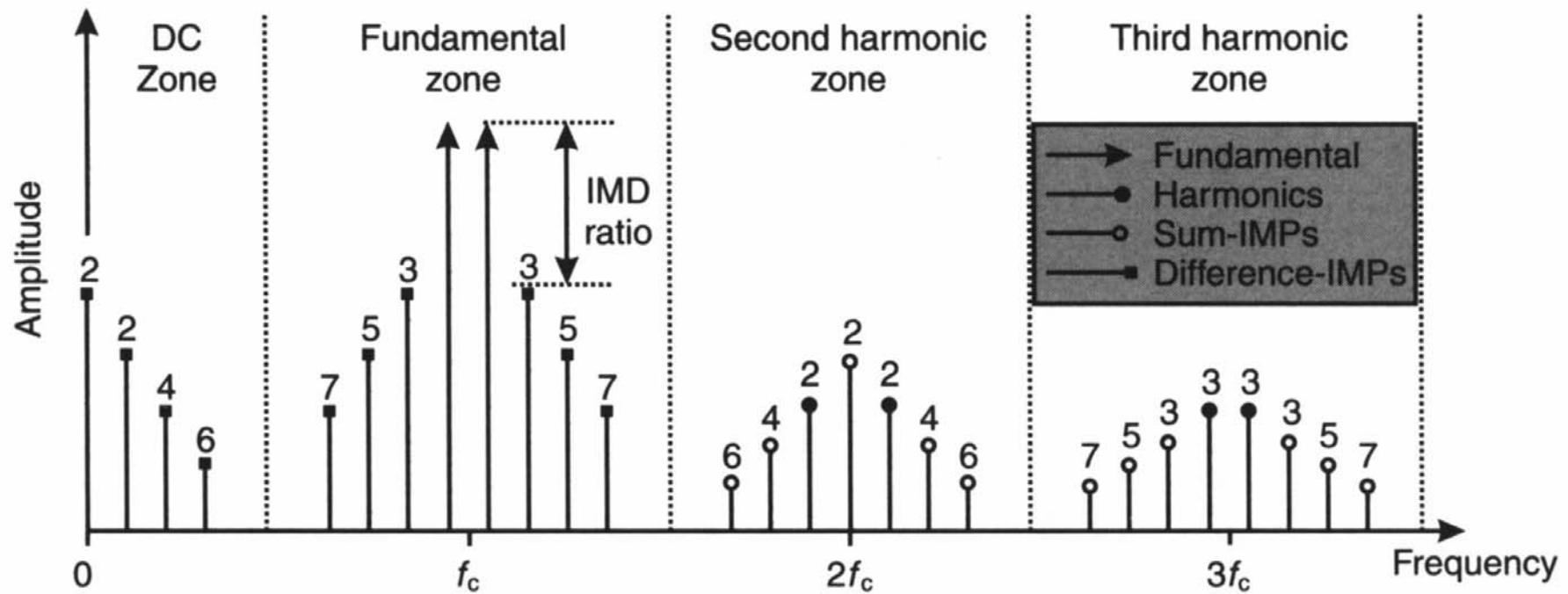


# Spectral Regrowth

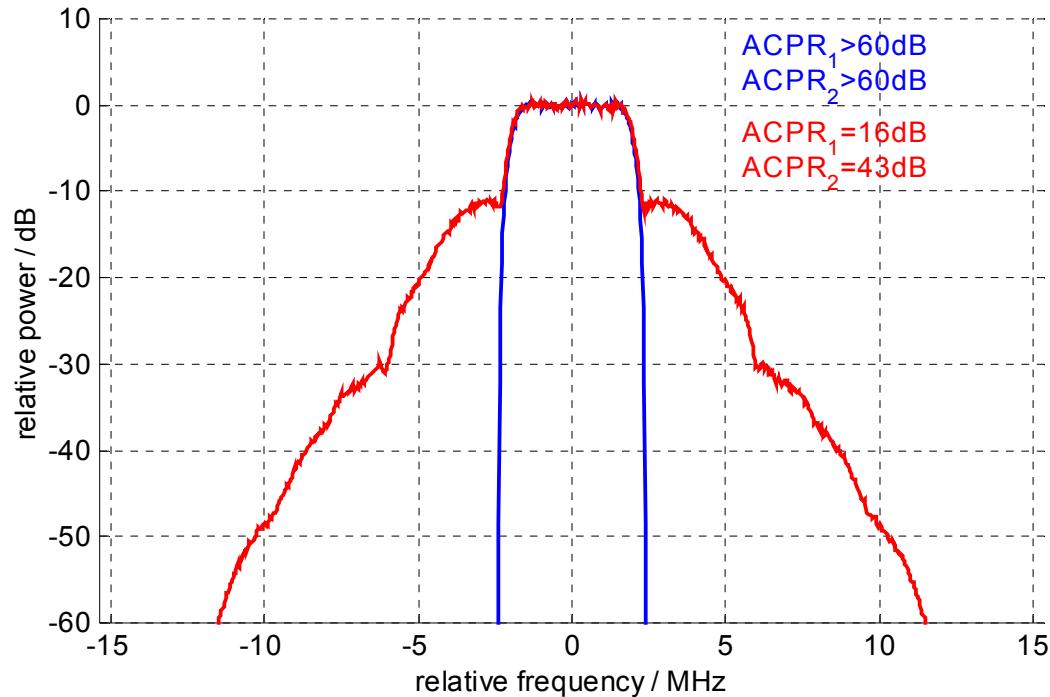


- Energy in adjacent Channels
- ACPR (Adjacent Channel Leakage Power Ratio) increases

# Reduced NPR (Noise Power Ratio)

- Input Signal

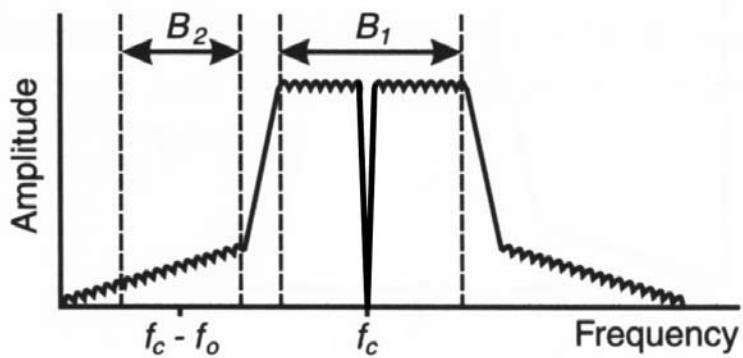


- Output Signal of Nonlinear Amplifier

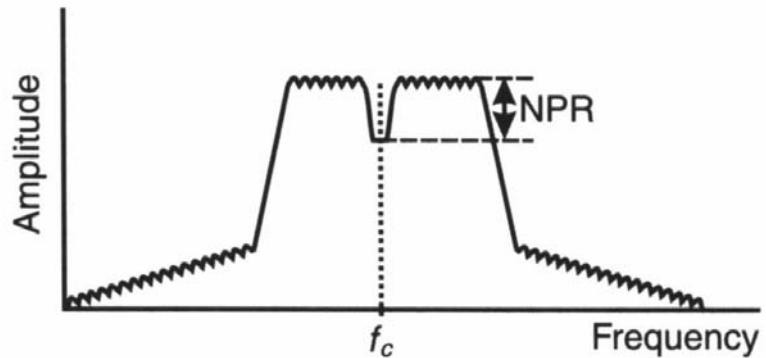


- Degradation of Inband SNR
- „Noisy“ Constellation

# Constellation Deformation

○ Input Signal

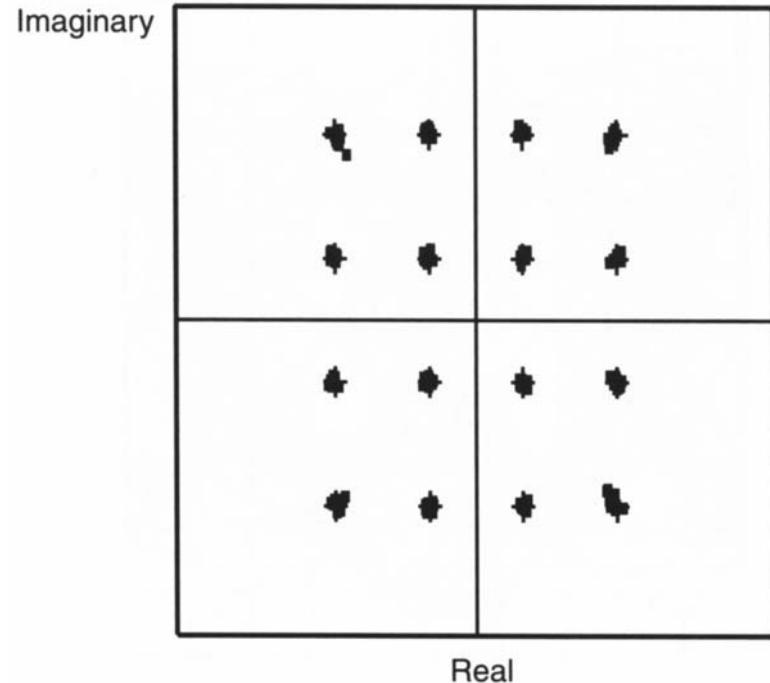

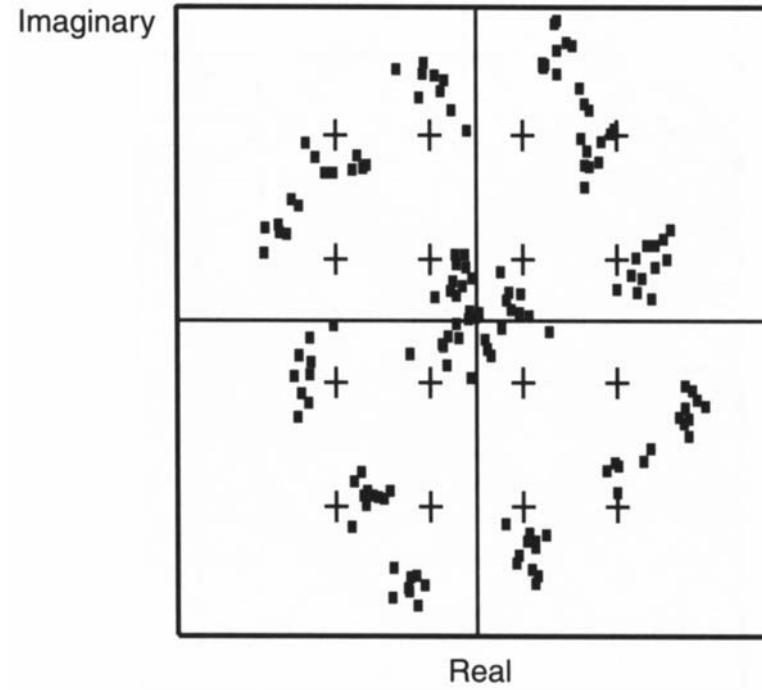
○ Output Signal of  
Nonlinear Amplifier  
(with Gain- and Phase-Distortion)


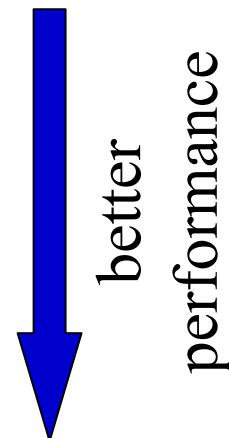
# Modeling of Nonlinearities



- with Memory-Effects
  - Volterra Series (=„Taylor Series with Memory“)

- without Memory-Effects
  - Saleh Model  $f(r) = \frac{\alpha_a r}{1 + \beta_a r^2}$      $g(r) = \frac{\alpha_\Theta r^2}{1 + \beta_\Theta r^2}$
  - Taylor Series
  - Blum and Jeruchim Model
  - AM/AM- and AM/PM-conversion



# AM/AM- and AM/PM-Conversion



## ○ GaAs-PA

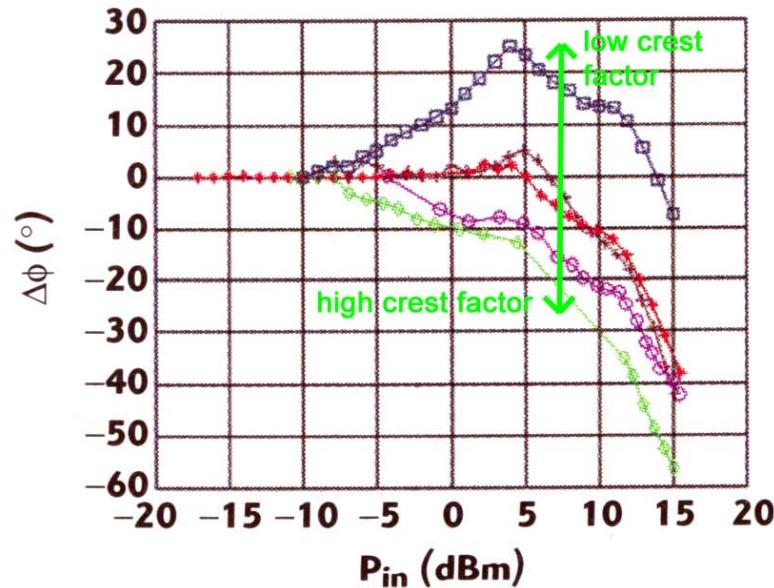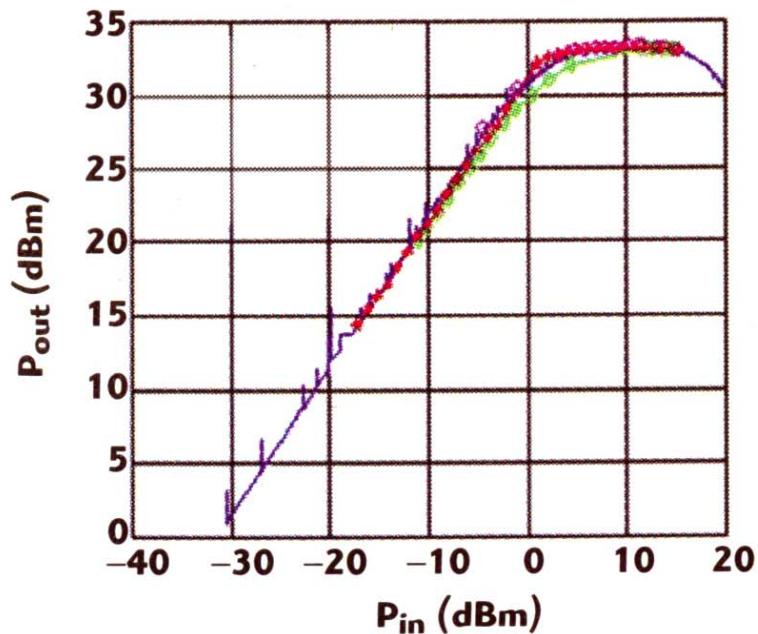

# AM/AM- and AM/PM-Conversion
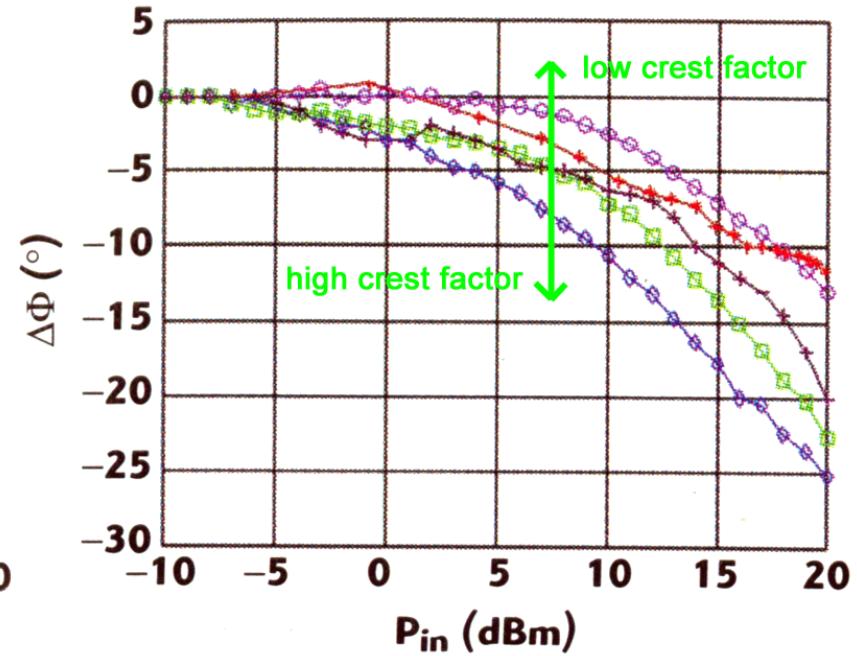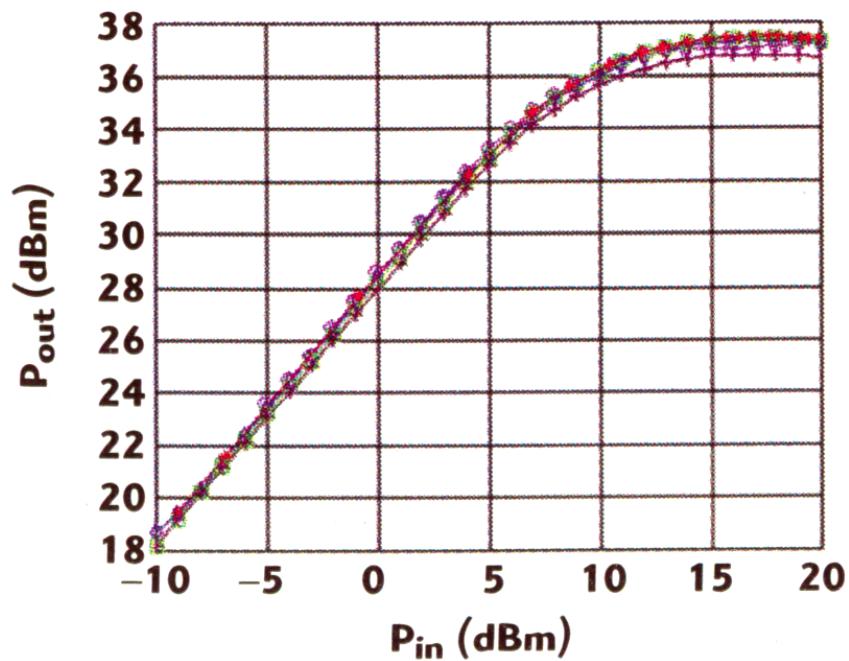
## ○ LDMOS-PA

◆ W-CDMA ONE USER    VNA  
■ GMSK                      SLOW RAMP  
+ SINGLE TONE (HF SCOPE)




# How to preserve Linearity?

- Backed-Off Operation of PA
  - Simplest Way to achieve Linearity
  
- Linearity improving Concepts
  - Predistortion
  - Feedforward
  - ...

# How to preserve Efficiency?


- Efficiency improving Concepts
  - Doherty
  - Envelope Elimination and Restoration
  - ...
  
- Linearity improving Concepts
  - Higher Linearity at constant Efficiency  
→ Higher Efficiency at constant Linearity

# Direct (RF) Feedback

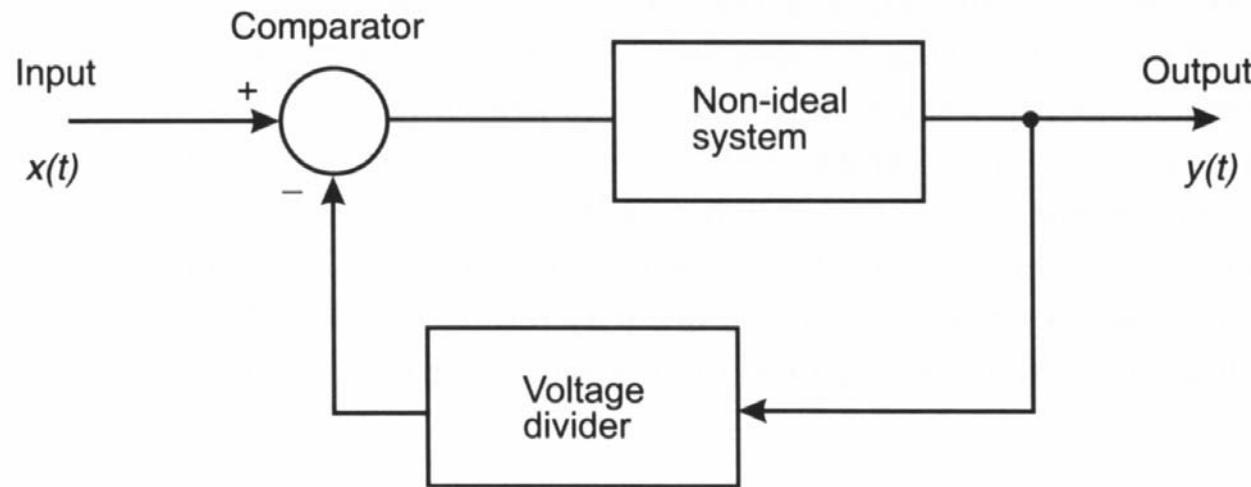


- Classical Method
- Decrease of Gain → Low Efficiency
- Feedback needs more Bandwidth than Signal
- Stability Problems at high Bandwidths

# Distortion Feedback

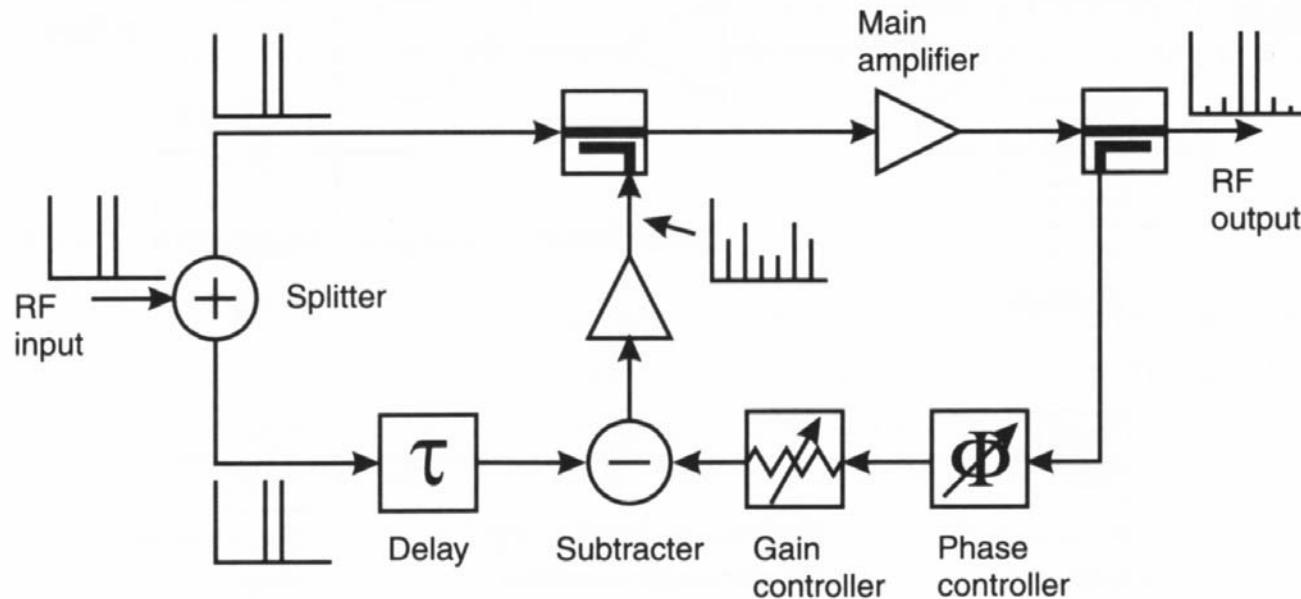


- Feedback of outband Products only
- Higher Gain than RF feedback
- Stability Problems due to Reverse Loop

# Feedforward

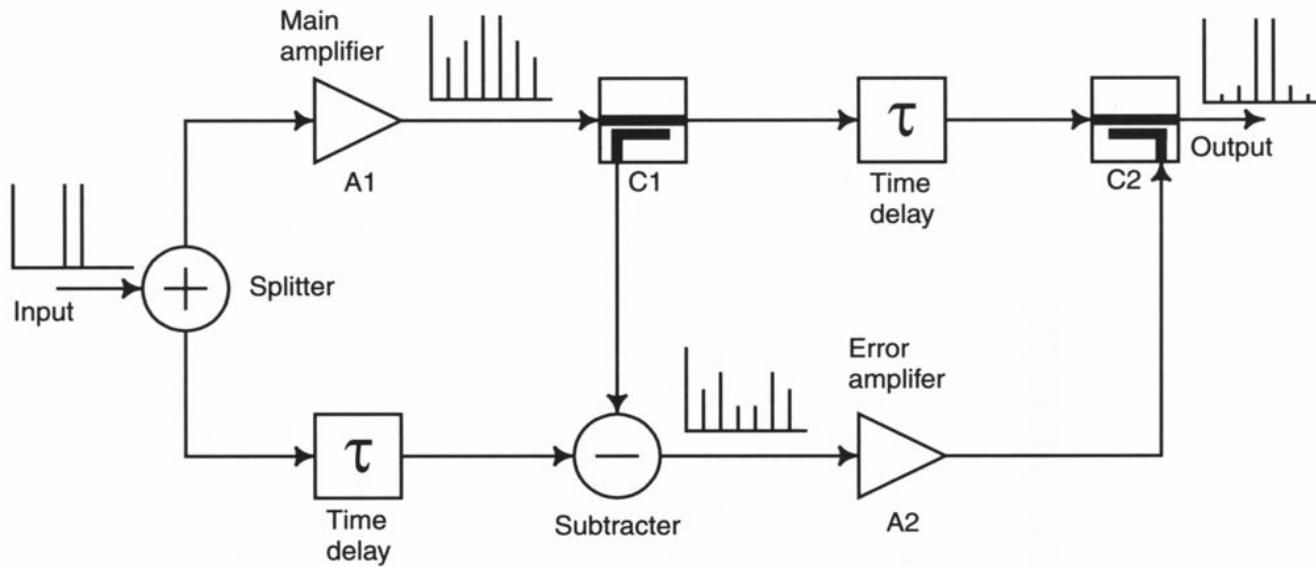


- Overcomes Stability Problem by forward-only Loops
- Critical to Gain/Phase-Imbalances
  - 0.5dB Gain Error  $\rightarrow$  -31dB Cancellation
  - 2.5° Phase Error  $\rightarrow$  -27dB Cancellation
- Well suited for narrowband application

# Cartesian Feedback

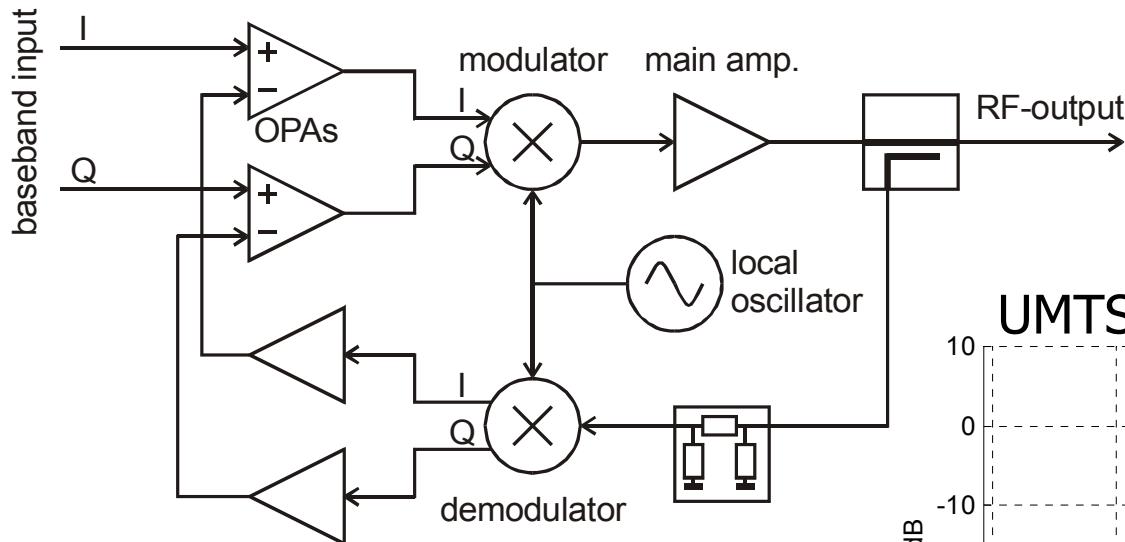


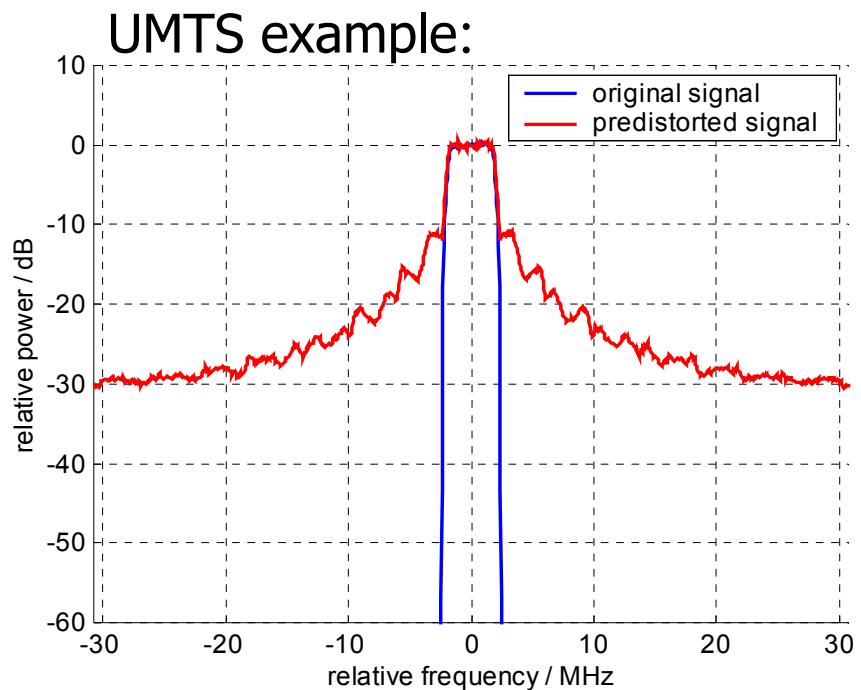- AM/AM- and AM/PM-correction
- High Feedback-Bandwidth
- Stability Problems



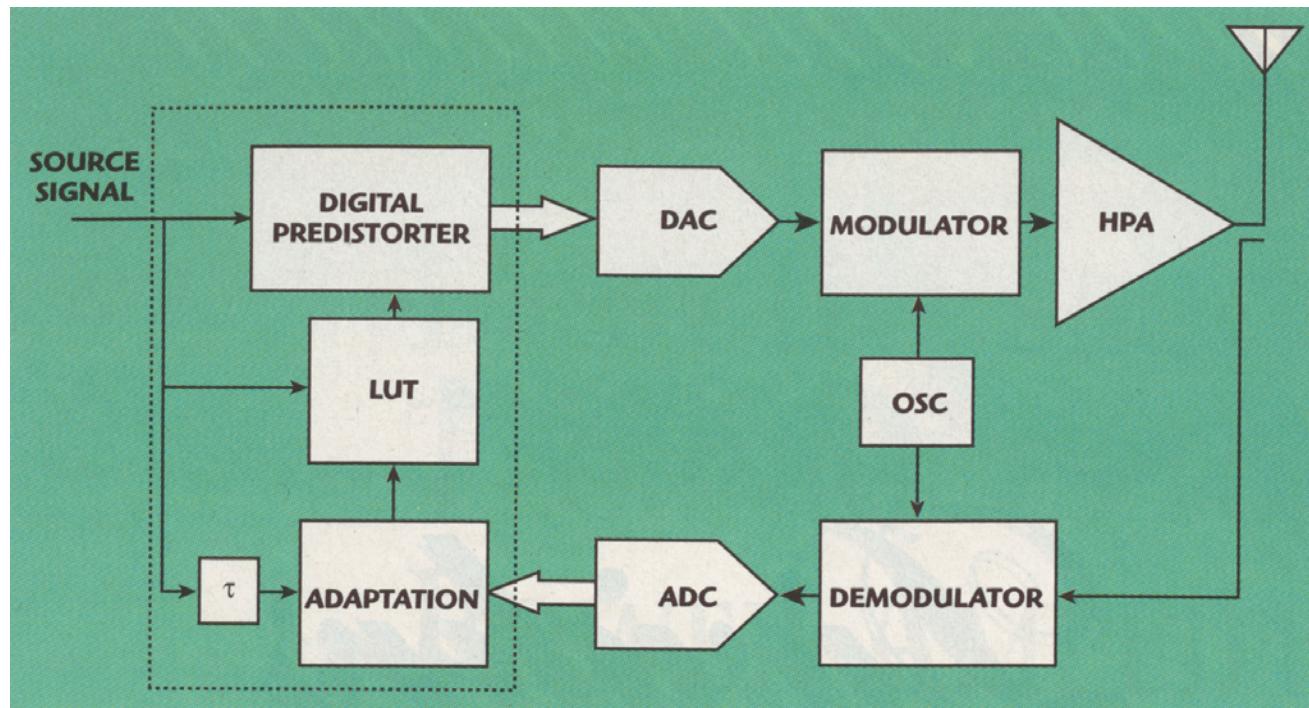
# Digital Predistortion

- Digital Implementation of „Cartesian Feedback“
- Additional ADCs, DSP Power, Oversampling needed
- Loop can be opened → no Stability Problems





# Analog Predistortion

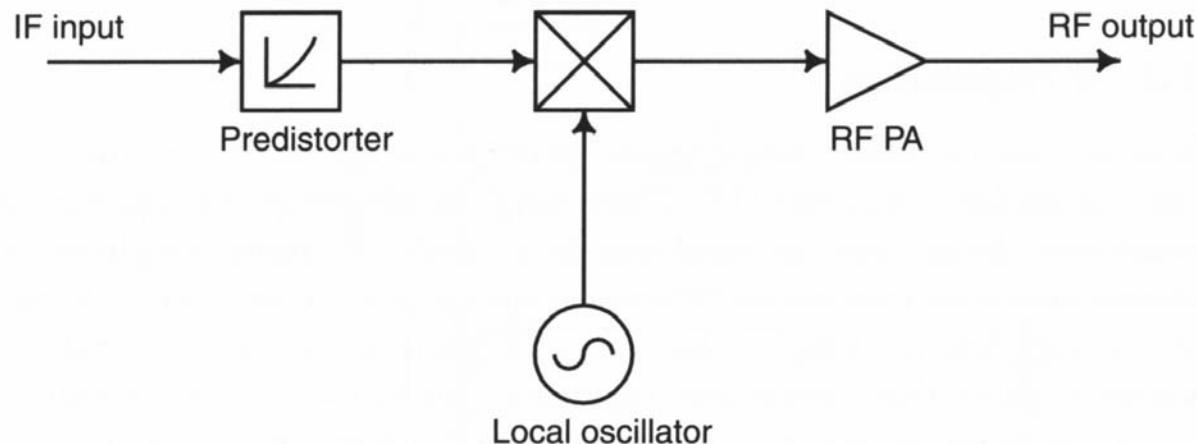


- Predistorter has inverse Function of Amplifier
- Leads to infinite Bandwidth (!)
- Hard to realize (accuracy)

# Analog Predistortion

## ○ Possible Realizations:

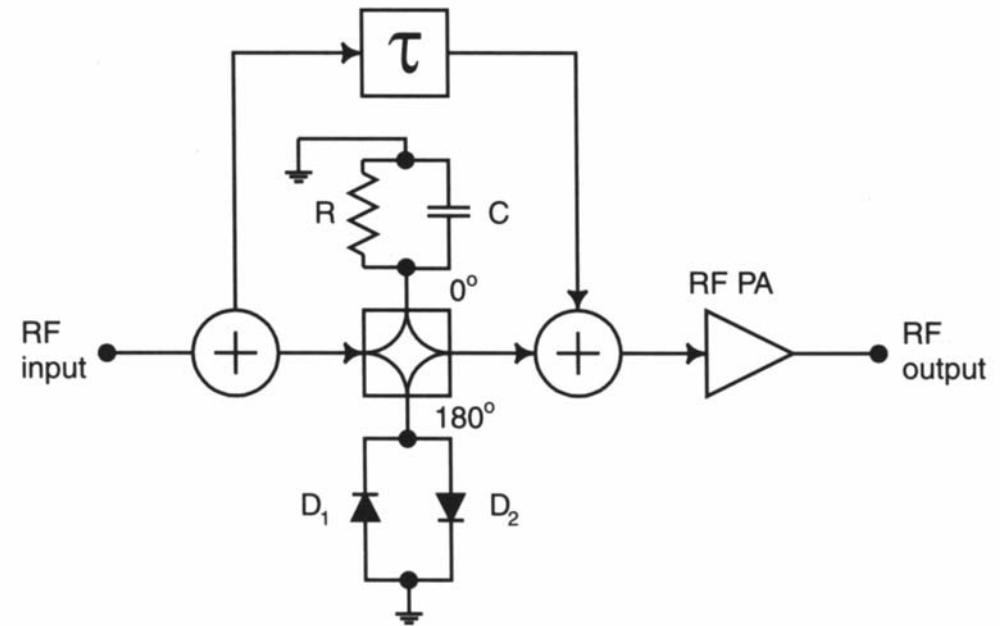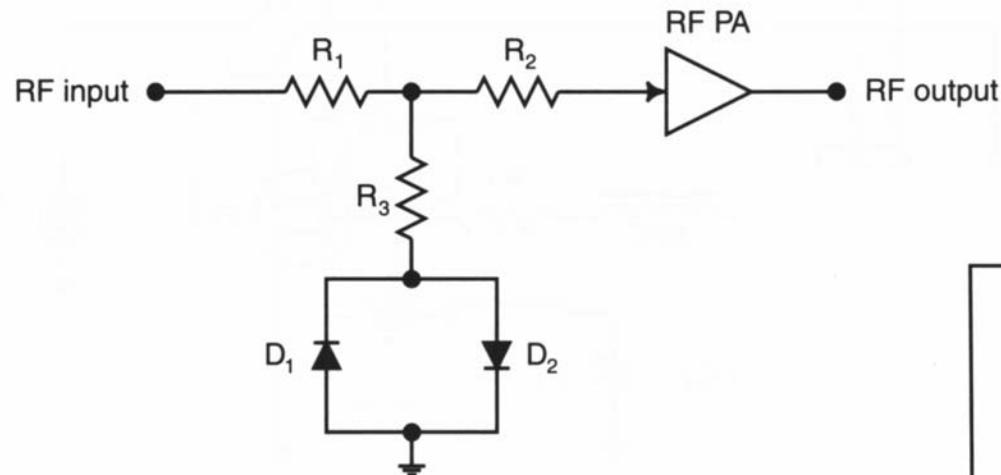

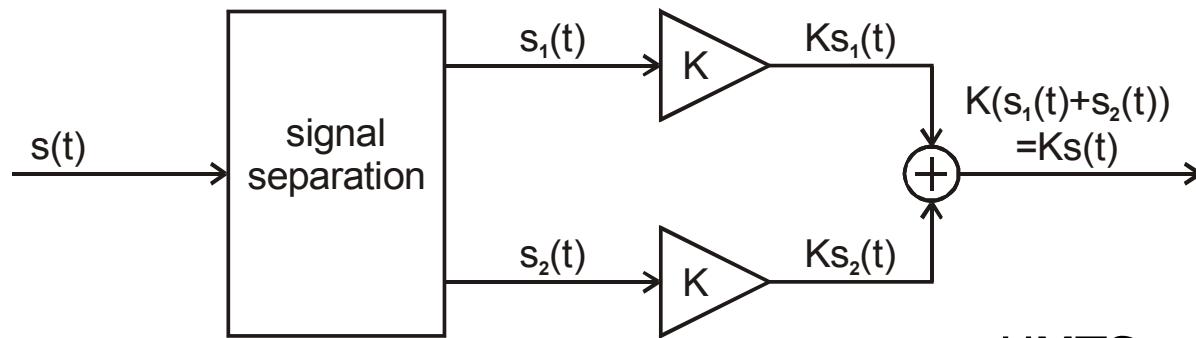
# LINC (Linear Amplification by Nonlinear Components)




- AM/AM- and AM/PM-correction
- Digital separation required (accuracy!)
- High Bandwidth, oversampling necessary
- Stability guaranteed

UMTS example:

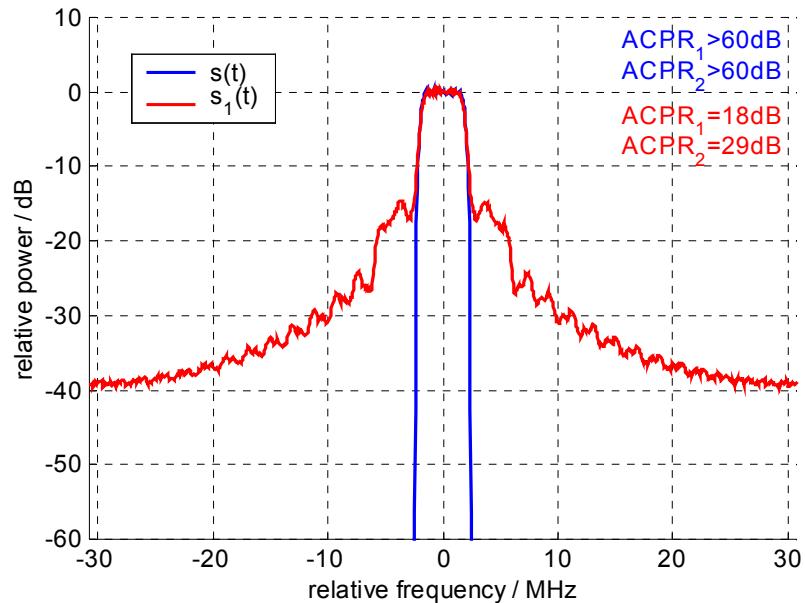

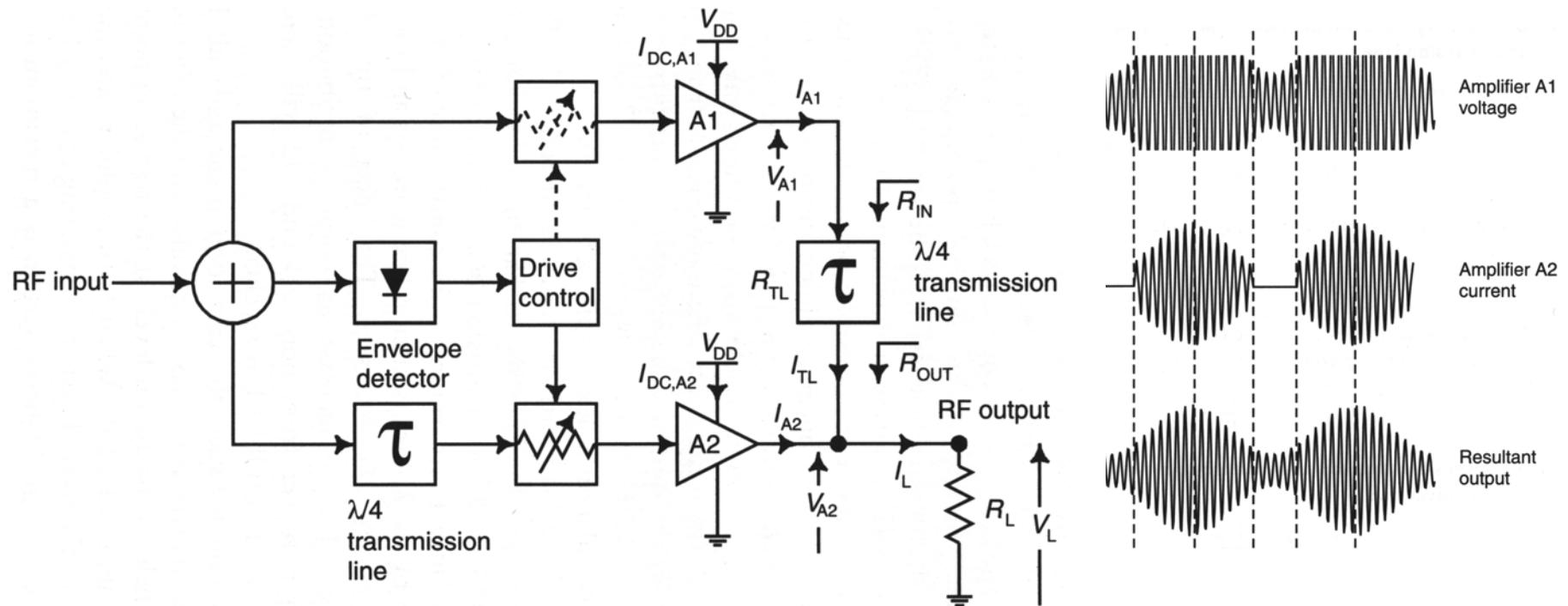
# Doherty Amplifier

- Auxiliary amplifier supports main amplifier during saturation
- PAE can be kept high over a 6dB range




# Doherty Amplifier

- Gain vs. Input Power

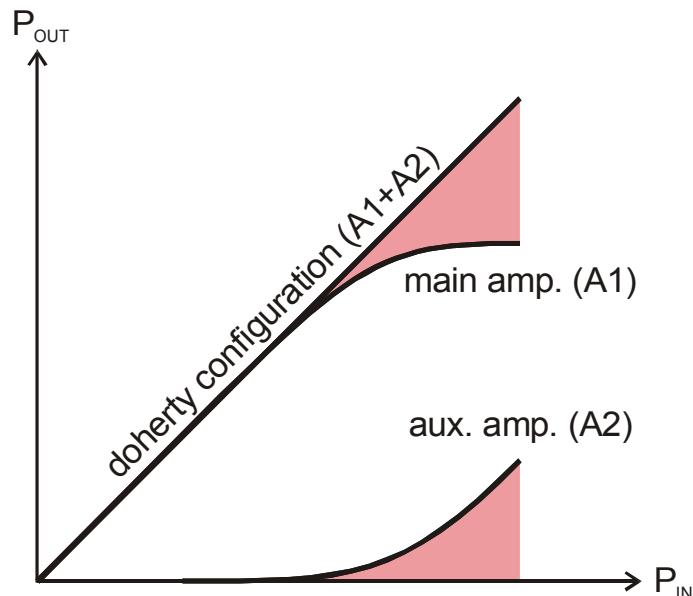


- Efficiency vs. Input Power

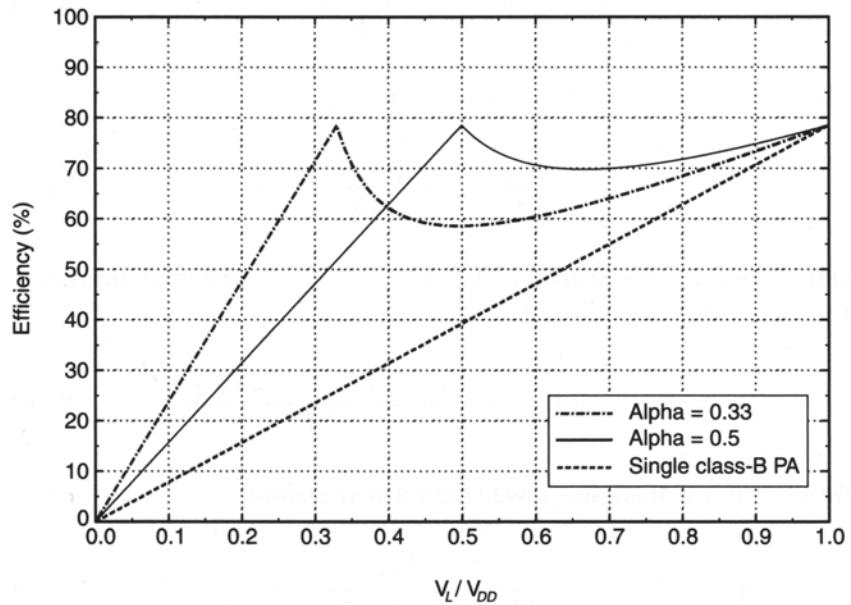

- No improvement of AM/AM- and AM/PM-distortion
- Behavior of auxiliary amplifier very hard (impossible) to realize
- Stability guaranteed
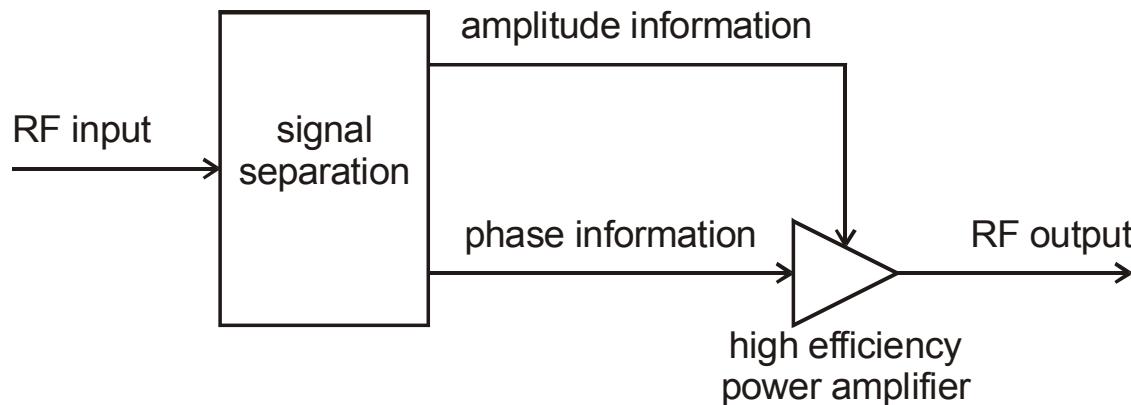
## EER (Envelope Elimination and Restoration)


- Separating phase and magnitude information
- Elimination of AM/AM-distortion
- Application of high-efficient amplifiers  
(independent of amplitude distortion)
- Stability guaranteed


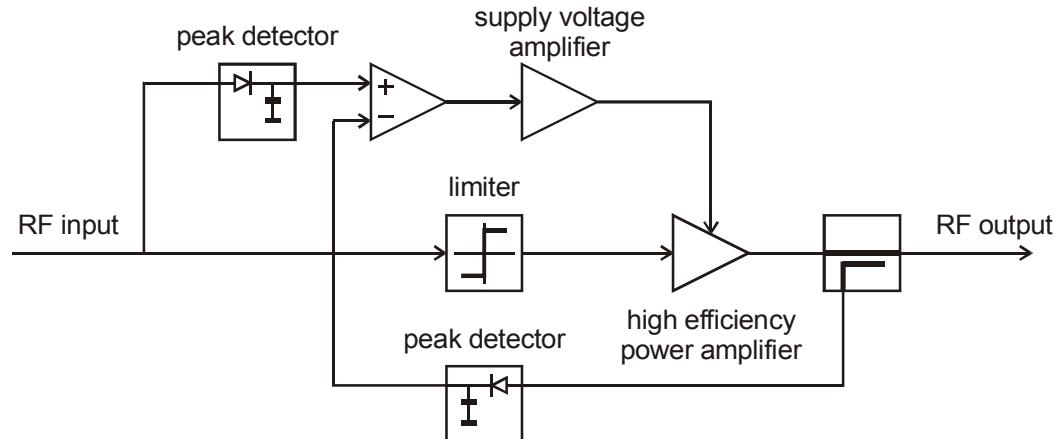
# EER (Envelope Elimination and Restoration)


- Analog realization

- Limiter hard to build
- Accuracy problems
- Feedback necessary





- Digital realization

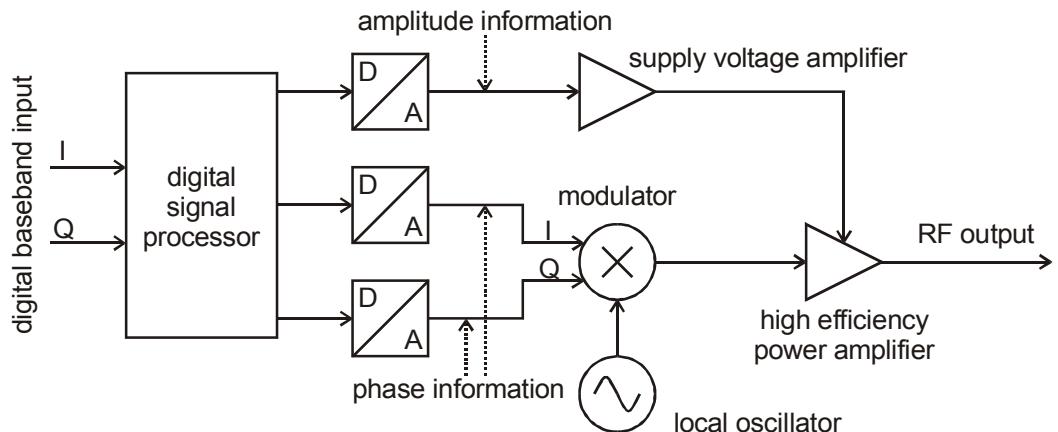- Oversampling + high D/A-conversion rates required
- High power consumption of DSP and D/A-converters
- Possible feedback elimination
- Compensation of AM/PM-distortion possible



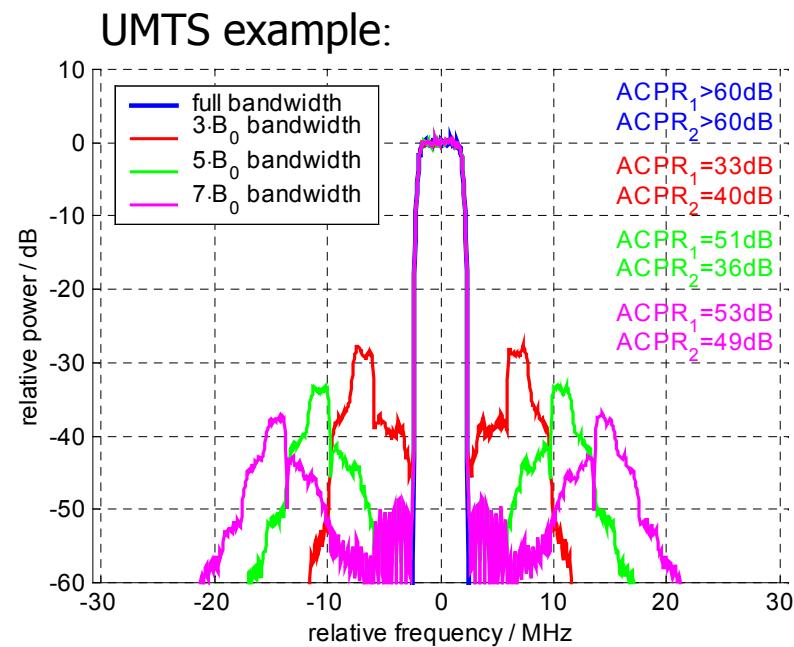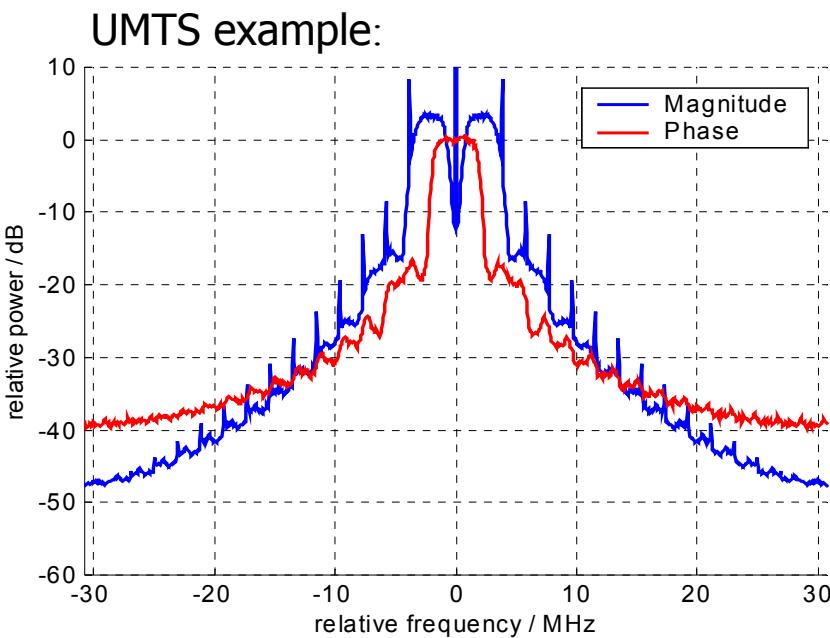
# EER (Envelope Elimination and Restoration)

- Bandwidth of Magnitude- and phase-signal have higher than transmit signal
- Five times (!) oversampling necessary to achieve standard requirements



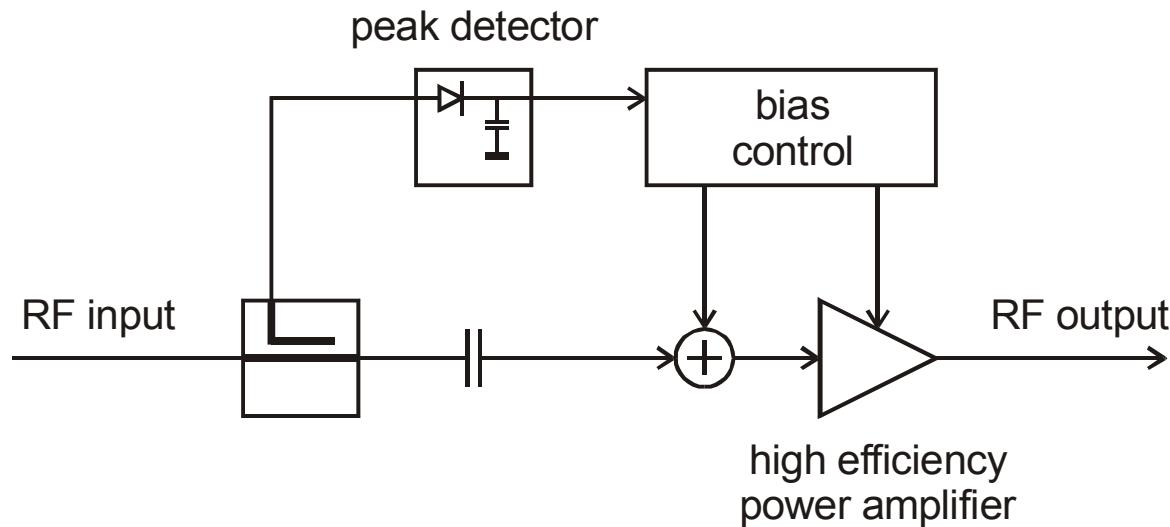
# Adaptive Bias

- Varying/Switching of Bias-Voltage depending on Input Power Level
- Selection of Operating Point with high PAE
- Applicably for nearly each type of Amplifier


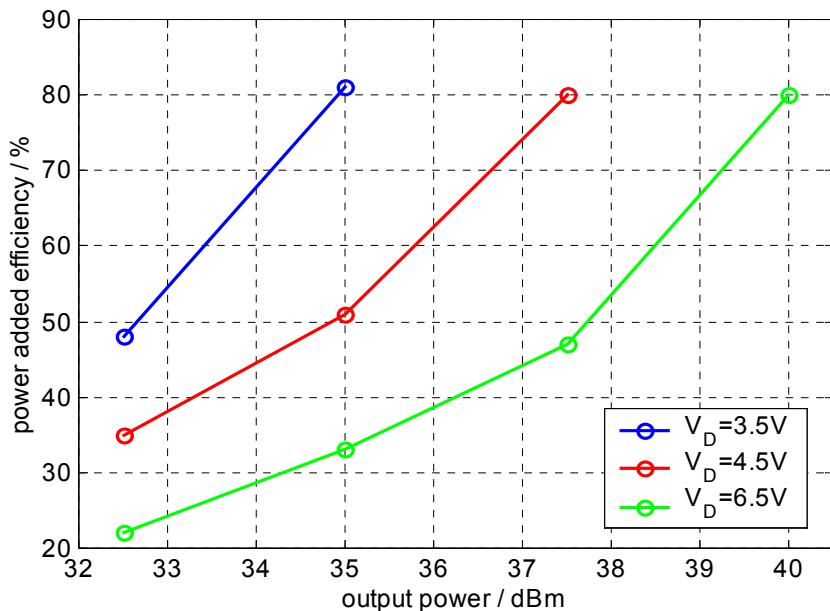
# Adaptive Bias

- Single tone PAE for switched  $V_{DD}$  with  $V_G$  kept constant



- Simply to implement Concept
- Stability guaranteed
- Possible problems:
  - DC-DC converter with high efficiency necessary
  - Possible Linearity Change (can increase and decrease) especially for HCAs

# Summary

- Digital Realization required to achieve Accuracy
- Problem of Stability for high Bandwidth Application
- Higher Bandwidths (Oversampling) necessary,  
depending on Order of IMD cancellation
- Predistortion gives best Results while keeping  
Efficiency high (valid for high Output Levels > 40dBm)

# Figure References

- F. Zavosh et al,  
“Digital Predistortion Techniques for RF Power  
Amplifiers with CDMA Applications”,  
Microwave Journal, Oct. 1999
  
- Peter B. Kenington,  
“High-Linearity RF Amplifier Design”,  
Artech House, 2000
  
- Steve C. Cripps,  
“RF Power Amplifiers for Wireless Communications”,  
Artech House, 1999

# Contact Information

## DI Markus Mayer

☎ +43-1-58801-35425

✉ markus.mayer@tuwien.ac.at

## DI Holger Arthaber

☎ +43-1-58801-35420

✉ holger.arthaber@tuwien.ac.at